

M1. (a) 450

*allow 1 mark for correct substitution,
ie $18 \times 10 \times 2.5$ provided no subsequent step shown*

2

- (b) (i) friction between child ('s clothing) and slide
*accept friction between two insulators
accept child rubs against the slide
accept when two insulators rub (together)*

1

causes electron / charge transfer (between child and slide)
*accept specific reference, eg electrons move onto / off the
child / slide
reference to positive electrons / protons / positive charge /
atoms transfer negates this mark
answers in terms of the slide being initially charged score
zero*

1

- (ii) all the charges (on the hair) are the same (polarity)
*accept (all) the charge/hair is negative / positive
accept it is positive/negative*

1

charges / hairs are repelling
both parts should be marked together

1

- (iii) charge would pass through the metal (to earth)
*accept metal is a conductor
accept metal is not an insulator
accept there is no charge / electron transfer
accept the slide is earthed
accept metals contain free electrons*

1

[7]

- M2.** (a) (i) Ends have charge
Which is opposite on each rod 2
- (ii) Attracts 1
- (b) (i) Repulsion 1
- (ii) Ends have same charge 1
- (c) Electrons move between cloth and rod
Where gather is negative
Where move from is positive 3

[8]

M3. (a) clothing and seat rub together
accept friction between clothing and seat

1

electrons transfer from seat to driver

or

electrons transfer from driver to seat

accept electrons transfer on its own if first mark scores

an answer in terms of rubbing, between clothing and seat

and charge transfer without mention of electrons gains 1 mark

an answer in terms of friction / rubbing and electron transfer without mention of clothing and seat gains 1 mark

1

(b) (i) how wet the air is affects charge (build up)
accept humidity affects charge

or

damp air is a better conductor

or

damp air has a lower resistance

do not accept fair test or as a control unless explained

1

(ii) No – it was only the lowest under these conditions
accept answer in terms of changing the conditions may change the results

or

No – there are lots of other materials that were not tested

or

Yes – the highest value for cotton is smaller than the lowest value for the other materials

do not accept results show that it is always less / smallest

1

[4]

M4. (a) 3rd box

The negative charge in the water is repelled by the rod and the positive charge is attracted.

1

(b) (i) friction between bottles and conveyor belt / (plastic) guides
accept bottles rub against conveyor belt / (plastic) guides

1

charge transfers between bottles and conveyor belt / (plastic) guides
accept specific reference
eg electrons move onto / off the bottles
reference to positive electrons / protons negates this mark

1

(ii) an atom that has lost / gained electron(s)
*do **not** accept a charged particle*

1

(iii) charge will not (easily) flow off the conveyor belt
accept the conveyor belt / bottle is an insulator / not a conductor
accept conveyor belt is rubber

1

[5]

M5. (a) electrons transfer / removed

*do **not** accept negatively charged atoms for electrons
this only scores if first mark given*

1

to the rod / from the cloth

*this does not score if there is reference to any original
charge on cloth or rod*

'it' refers to the rod

*accept negative charge transfer to rod / removed from cloth
for 1 mark*

transfer of positive charge / positive electrons scores zero

1

(b) (i) rods / charges repel

1

creating downward / extra force (on the balance)

accept pushing (bottom) rod downwards

do not accept increasing the weight / mass

charges attracting scores zero

1

(ii) the (repulsion) force increases as the distance between the charges decreases

*accept there is a negative correlation between (repulsion)
force and distance between charges or (repulsion) force and
distance between charges are inversely proportional*

for both marks

examples of 1 mark answers

force increases as distance decreases

force and distance are inversely proportional

negative correlation between force and distance

repels more as distance decreases

*if given in terms of attracting or attraction force this mark
does not score*

2

[6]

M6. (a) (i) friction between the beads and pipe
accept beads rub against the pipe

1

(cause) electrons to transfer
accept electrons are lost/gained
*do **not** accept negatively charged atoms for electrons*
3rd mark point only scores if 2nd mark scores

1

from the pipe
*do **not** accept from the (negatively) charged pipe*
or to the beads
*do **not** accept to the (positively) charged beads*
accept negative charge transfer to the beads for 1 mark
provided 2nd or 3rd marking point not awarded
mention of positive charge transfer negates last 2 marking
points

1

(ii) volume of beads
accept (75)cm³
or
length of pipe
accept use the same pipe

or
speed the beads are poured
poured the same way is insufficient
or
angle of pipe

1

(b) (i) the larger the beads the less charge
*do **not** accept inversely proportional*
negative correlation is insufficient

1

(ii) (total) charge decrease

results would be lower/smaller would be insufficient

1

beads in contact with pipe (walls) for less time
accept less contact (between beads and pipe)
accept beads in pipe for less time

or

smaller surface area (to rub against)
accept less pipe to rub against
less friction is insufficient

1

- (c) (i) (pumping very) fine powders
reason only scores if (very) fine powders given

greater charge (build up)
accept more static (electricity)
accept an answer that correctly relates back to the experimental data

or higher pd/voltage **or** greater energy
accept larger surface area to volume (ratio)

1

- (ii) idea of earthing (the pipe)
accept use metal pipes
*do **not** accept use larger particles*

1

- (d) to compare (the relative risks)
fair test is insufficient
you can only have one independent variable is insufficient
or different conditions change the MIE value
accept different conditions change the results
*do **not** accept avoid bias*

1

[10]

M7.

(a) 3rd box

The negative charge in the water is repelled by the rod and the positive charge is attracted to the rod.

1

(b) (i) friction between bottles and conveyor belt / (plastic) guides
accept bottles rub against conveyor belt / (plastic) guides

1

charge transfers between bottles and conveyor belt / (plastic) guides
accept specific reference eg electrons move onto / off the bottles
reference to positive electrons / protons negates this mark

1

(ii) (the atom) loses or gains one (or more) electrons


1

(iii) charge will not (easily) flow off the conveyor belt / bottles
accept the conveyor belt / bottles is an insulator / not a conductor accept conveyor belt is rubber

1

[5]

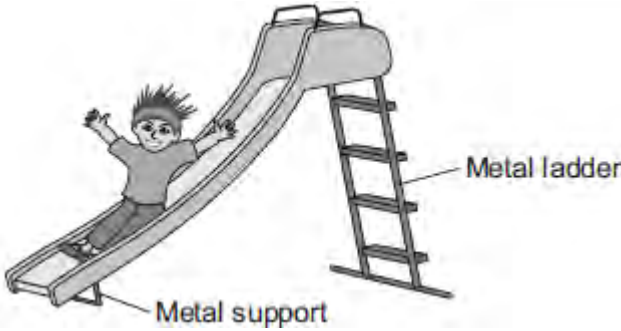Q1. The figure below shows a slide in a children's playground.



(a) A child of mass 18 kilograms goes down the slide.

The vertical distance from the top to the bottom of the slide is 2.5 metres.

Calculate the decrease in gravitational potential energy of the child sliding from the top to the bottom of the slide.

Gravitational field strength = 10 N / kg

.....
.....
.....

Decrease in gravitational potential energy = J

(2)

(b) The slide is made of plastic.

(i) The child becomes electrically charged when he goes down the slide.

Explain why.

.....
.....
.....
.....

(2)

(ii) Going down the slide causes the child's hair to stand on end.

What conclusion about the electrical charge on the child's hair can be made

from this observation?

.....
.....

Give a reason for your answer.

.....
.....

(2)

(iii) Why would the child **not** become electrically charged if the slide was made from metal?

.....
.....


(1)

(Total 7 marks)

Q2. A pupil did an experiment following the instructions below.

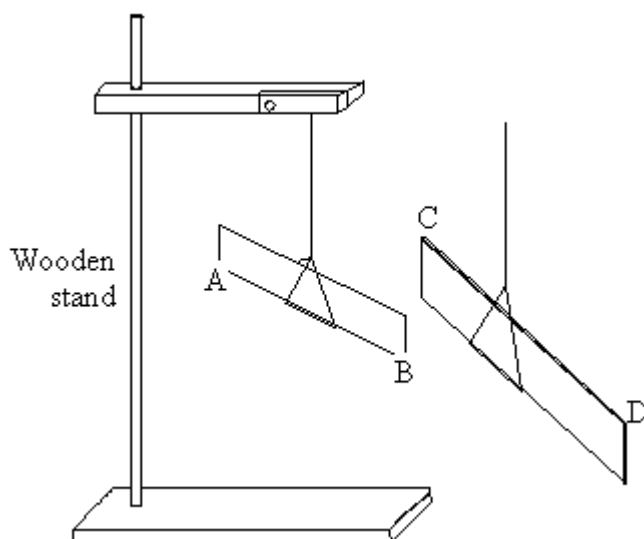1. Take a polythene rod (AB), hold it at its centre and rub both ends with a cloth.
2. Suspend the rod, without touching the ends, from a stand using a stirrup and nylon thread.
3. Take a perspex rod (CD) and rub it with another cloth.
4. Without touching the ends of the perspex rod bring each end of the perspex rod up to, but without touching, each end of the polythene rod.
5. Make notes on what is observed.

The diagram below shows how the apparatus is to be set up.



(a) When end C was brought near to end B they attracted each other.

(i) Explain why they attracted each other.

.....
.....

(ii) What would happen if end C were brought near end A?

.....

(3)

(b) The experiment was repeated with two polythene rods.

(i) Describe what you would expect the pupil to observe as the end of one rod was brought near to the end of the other.

.....
.....

(ii) Explain your answer.

.....
.....

(2)

(c) Explain, in terms of electron movement, what happened as the rods were rubbed with the cloths.

.....
.....
.....
.....
.....

(3)

(Total 8 marks)

Q3. During car journeys, the driver will often become electrostatically charged.

This is more noticeable on dry days than on damp, humid days.

(a) Explain what happens to cause the driver to become charged.

.....
.....
.....
.....

(2)

(b) Scientists were asked to find out whether the build-up of charge on the driver depends on the type of material used to make the driver's clothes. The results of the investigation are given in the table.

Material	Humidity	Temperature in °C	Charge on the driver in millicoulombs
Nylon	48%	18	3.0 to 3.2
Wool	48%	18	2.4 to 2.5
Cotton	48%	18	1.4 to 1.7

Humidity is a measure of how much water vapour the air can hold.

(i) Why was it important that the scientists controlled the humidity?

.....
.....

(1)


(ii) Does the data in the table show that the charge on the driver would always be less if they were to wear cotton clothing?

Give a reason for your answer.

.....

.....
(1)
(Total 4 marks)

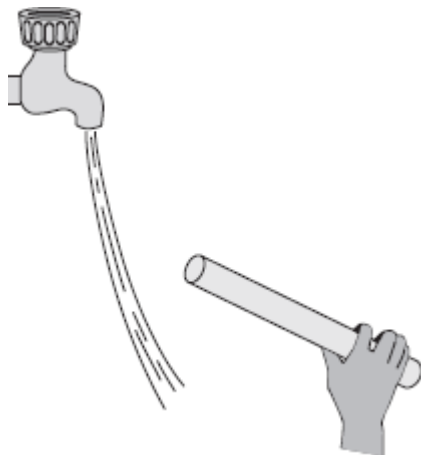- Q4.** (a) The diagram shows a negatively charged plastic rod held close to a thin stream of water. The water is attracted towards the rod.



Which **one** of the following statements explains what is happening to the charge in the water?

Tick (✓) **one** box.

The positive and the negative charges in the water are attracted to the rod.

The positive and the negative charges in the water are repelled by the rod.


The negative charge in the water is repelled by the rod and the positive charge is attracted.

The negative charge in the water is attracted by the rod and the positive charge is repelled.

(1)

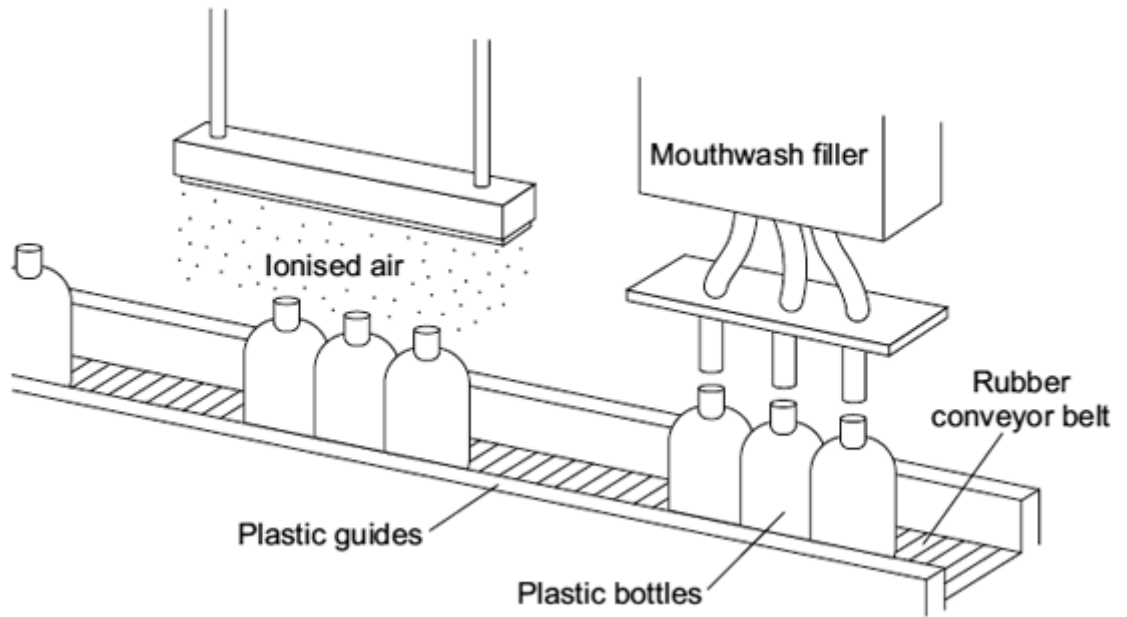- (b) A company that produces bottles of mouthwash found a problem with the automatic filling system.

As the bottles go towards the filler, they move around on the conveyer belt and become electrostatically charged. This causes the stream of mouthwash to move sideways, missing the open top of the bottle.



The company came up with a solution to the problem. Before the bottles reach the filler, they pass through a stream of ionised air. The ions in the air neutralise the charge on the bottles.

(i) Explain why the plastic bottles become charged.

.....

.....

.....

.....

(2)

(ii) What is an ion?

.....

.....

(1)


(iii) Earthing the conveyor belt with a conducting wire would not have solved this problem.

Give a reason why.

.....

.....
(1)
(Total 5 marks)

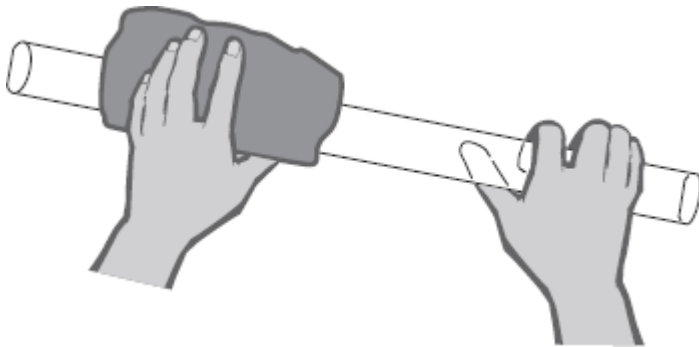Q5.(a) The diagram shows a polythene rod being rubbed with a woollen cloth.



The polythene rod becomes negatively charged.

Explain how this happens.

.....


.....

.....

.....

(2)

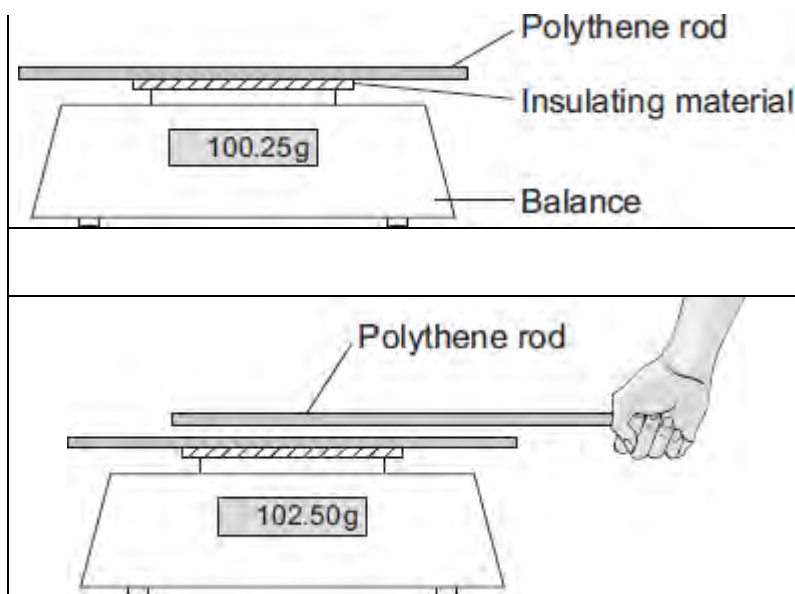- (b) A student put the charged polythene rod on to a balance. The rod was separated from the metal pan of the balance by a thin block of insulating material. The student then held a second charged polythene rod above, but **not** touching, the first rod. The reading on the balance increased.



- (i) Explain why the reading on the balance increases.

.....
.....
.....
.....

(2)

- (ii) The student observed that the nearer the two rods are to each other, the bigger the increase in the balance reading.


What should the student conclude from this observation?

.....
.....
.....
.....

(2)

(Total 6 marks)

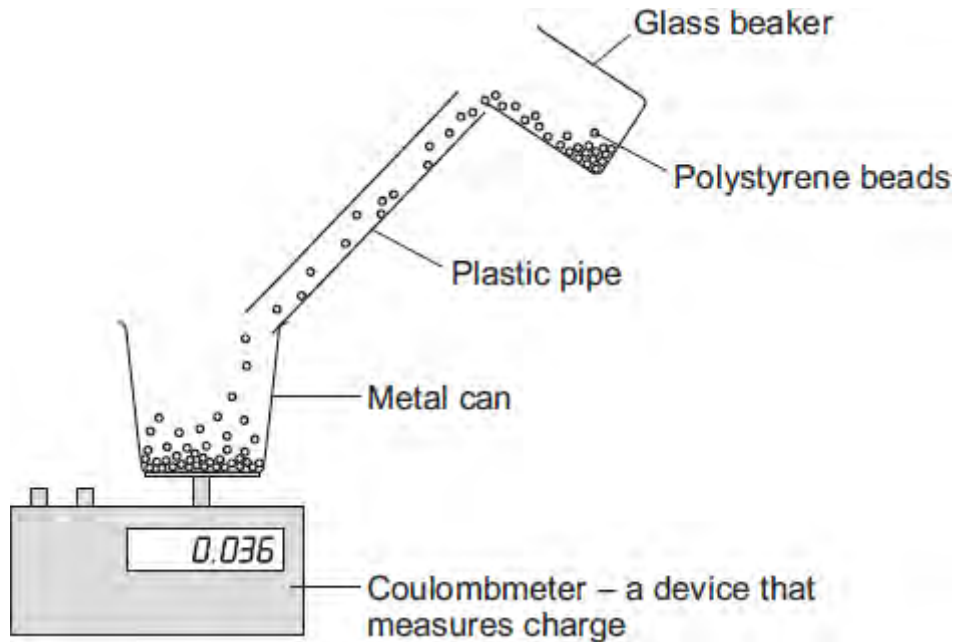Q6.(a) Fine powders poured through a pipe can become charged. The diagram shows the apparatus used by a student to investigate this effect.



The student poured 75 cm³ of polystyrene beads down the pipe. The beads fell into a metal can and the charge on them was measured directly using a coulombmeter.

The student repeated this twice more, but each time used 75 cm³ of beads of a different size.

- (i) When they fell through the pipe, the polystyrene beads became negatively charged.

Explain how this happened.

.....

.....

.....

.....

.....

.....

(3)

- (ii) Give **one** control variable in the student's investigation.

.....

.....

(1)

(b) The results obtained by the student are shown in the table.

Diameter of polystyrene beads in mm	Charge in microcoulombs
1.0	0.080
2.0	0.044
3.0	0.012

(1 000 000 microcoulombs = 1 coulomb)

(i) Describe the connection between the size of the polystyrene beads and the total charge on the beads.

.....
.....

(1)

(ii) Explain how these results might be different if the student had used a shorter pipe.

.....
.....
.....
.....

(2)

(c) In industry, powders are often pumped through pipes. If the static charge caused a spark, the powder could ignite and cause an explosion.

(i) Is an explosion more likely to happen when pumping very fine powders or when pumping powders that consist of much larger particles?

.....

Give a reason for your answer.

.....
.....

(1)

(ii) Suggest **one** way that the risk of an explosion could be reduced.

.....
.....

(1)

(d) The table gives the minimum ignition energy (MIE) value for a number of fine powders.
The MIE is the minimum amount of energy required to cause a fine powder to ignite.

Type of powder	MIE in millijoules
Coal dust	60.00
Aluminium powder	10.00
Cornstarch dust	0.30
Iron powder	0.12

The MIE values for different substances are all measured in the same way and under the same conditions of pressure and temperature.


Why is this important?

.....
.....

(1)

(Total 10 marks)

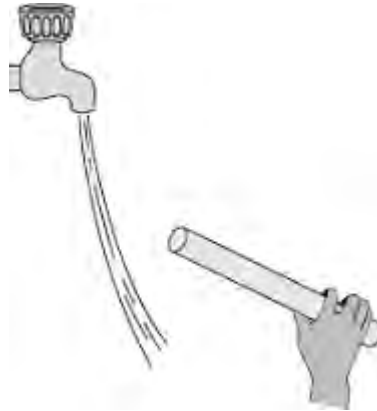Q7.(a) The diagram shows a negatively charged plastic rod held near to a thin stream of water. The water is attracted towards the rod.



Which **one** of the following statements explains what is happening to the charge in the water?

Tick (✓) **one** box.

The positive and the negative charges in the water are attracted to the rod.

The positive and the negative charges in the water are repelled by the rod.


The negative charge in the water is repelled by the rod and the positive charge is attracted to the rod.

The negative charge in the water is attracted to the rod and the positive charge is repelled by the rod.

(1)

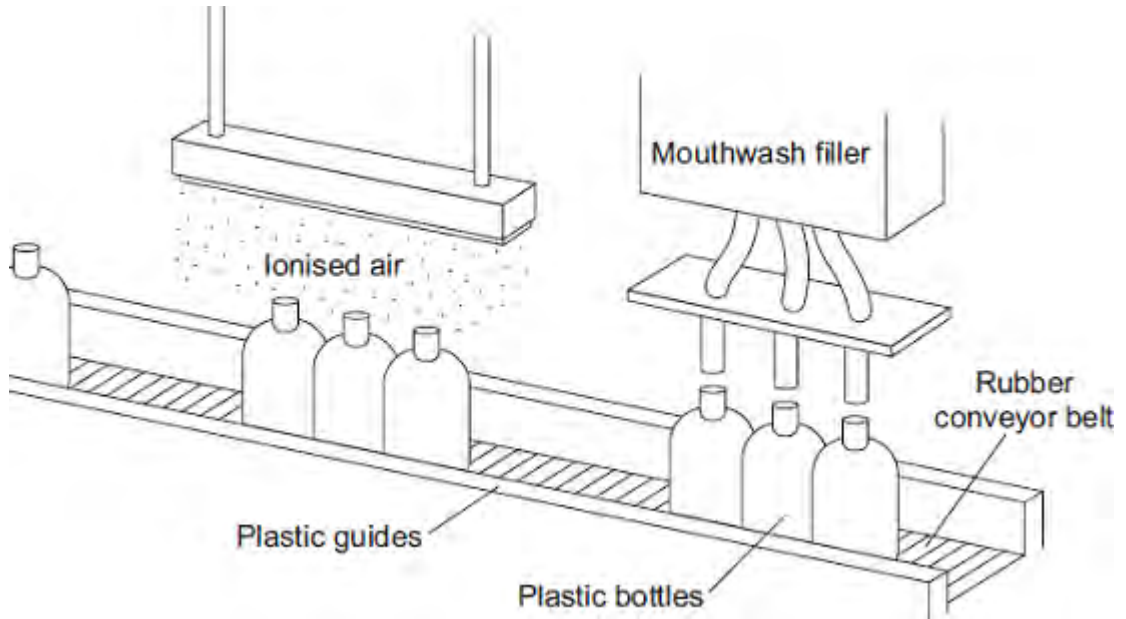(b) A company that produces bottles of mouthwash found a problem with the automatic filling system.

As the bottles go towards the filler, the bottles move around on the conveyor belt and become electrostatically charged. This causes the stream of mouthwash to move sideways, missing the open top of the bottle.



The company came up with an answer to the problem. Before the bottles reach the dfiller, the bottles pass through a stream of ionised air. The ions in the air neutralise the charge on the bottles.

- (i) Explain why the plastic bottles became charged.

.....

.....

.....

.....

(2)

- (ii) What happens to the structure of an atom to change the atom into an ion?

.....

.....

(1)

- (iii) Earthing the conveyor belt with a conducting wire would not have solved this problem.
Give a reason why.

.....

.....

(1)
(Total 5 marks)

M1. (a) current that is always in the same direction 1

(b) total resistance = 30 (Ω) 1

$$V = 0.4 \times 30$$
1

12 (V) 1

*allow 12 (V) with no working shown for 3 marks
an answer of 8 (V) or 4 (V) gains 2 marks only*

(c) $P = 0.4 \times 12 = 4.8$ 1

5 (W) 1

*allow 5 (W) with no working shown for 2 marks
allow 4.8 (W) with no working shown for 1 mark*

[6]

M2. (a) (i) 15 1

(ii) 4.5 or their (a)(i) x 0.3 correctly calculated
*allow 1 mark for correct substitution, ie 0.3 x 15/their (a)(i),
provided no subsequent step* 2

(ii) decrease 1

(b) **Y**
*accept any correct indication
reason only scores if Y is chosen
accept voltage for p.d.* 1

(only one that) shows a direct current / p.d.
or
a battery / cell gives a direct current
accept both X and Z are a.c.

or
a battery/cell gives a constant current/p.d.
*accept it's a constant current/p.d.
it is not changing is insufficient* 1

[6]

M3. (a) (i) 50 (Hz) 1

(ii) 2760 (W) 1

(b) 12
allow 1 mark for correct substitution, ie 2400/200
or
allow 1 mark for 2760/230 provided no subsequent step shown 2

amps 1

(c) the charge is directly proportional to the time switched on for
accept for 1 mark the longer time (to boil), the greater amount of charge
or positive correlation
or they are proportional 2

[7]

M4. (a) $25(\Omega)$

1

(b) (i) $2(\text{V})$

allow 1 mark for showing a correct method, ie 6 / 3


2

(ii) equal to

1

[4]

M5.(a)

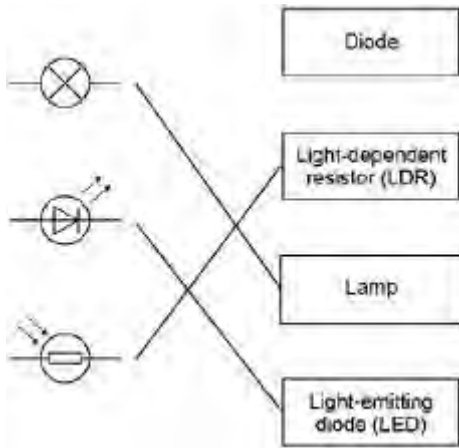

allow 1 mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong

3

(b) (i) half

1

(ii) 3(V)

1

(iii) V_1

1

(c) (i) potential difference / voltage of the power supply
 accept the power supply
 accept the voltage / volts
 accept number of cells / batteries
 accept (same) cells / batteries
 do not accept same ammeter / switch / wires

1

(ii) bar drawn – height 1.00A
 ignore width of bar
 allow 1 mark for bar shorter than 3rd bar

2

(iii) as the number of resistors increases the current decreases

1

[10]

M6.(a)	battery, lamp and ammeter connected in series with variable resistor	1
	voltmeter in parallel with (filament) lamp	1
(b)	<p>Level 2 (3–4 marks): A detailed and coherent description of a plan covering all the major steps is provided. The steps are set out in a logical manner that could be followed by another person to obtain valid results.</p> <p>Level 1 (1–2 marks): Simple statements relating to relevant apparatus or steps are made but they may not be in a logical order. The plan would not allow another person to obtain valid results.</p> <p>0 marks: No relevant content</p> <p>Indicative content</p> <ul style="list-style-type: none"> • ammeter used to measure current • voltmeter used to measure potential difference • resistance of variable resistor altered to change current in circuit or change potential difference (across filament lamp) • resistance (of filament lamp) calculated or $R=V / I$ statement • resistance calculated for a large enough range of different currents that would allow a valid conclusion about the relationship to be made 	4
(c)	(as current increases) resistance increases (at an increasing rate)	1
(d)	any value between 6.3 and 6.9 (Ω)	1
(e)	A: Filament lamp	1
	B: Resistor at constant temperature	

1

C: Diode

1

[11]

M7.(a) (i) any **six** from:

- switch on
- read both ammeter and voltmeter
allow read the meters
- adjust variable resistor to change the current
- take further readings
- draw graph
- (of) V against I
allow take mean
- $R = V / I$
allow take the gradient of the graph

6

(ii) resistor would get hot if current left on

1

so its resistance would increase

1

(iii) 12 (V)

0.75 × 16 gains 1 mark

2

(iv) 15 (Ω)

1

16 is nearer to that value than any other

1

(b) if current is above 5 A / value of fuse

1

fuse melts

allow blows / breaks


*do **not** accept exploded*

1

breaks circuit

1
[15]

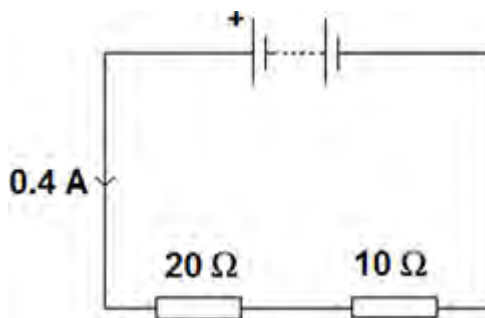Q1. An electrical circuit is shown in the figure below.



(a) The current in the circuit is direct current.

What is meant by direct current?

Tick **one** box.

Current that continuously changes direction.

Current that travels directly to the component.

Current that is always in the same direction.

(1)

(b) The equation which links current, potential difference and resistance is:

$$\text{potential difference} = \text{current} \times \text{resistance}$$

Calculate the potential difference across the battery in the circuit in the figure above.

.....
.....

$$\text{Potential difference} = \dots\dots\dots \text{ V}$$

(3)

(c) The equation which links current, potential difference and power is:

$$\text{power} = \text{current} \times \text{potential difference}$$

Calculate the power output of the battery in the figure above.

Give your answer to one significant figure.


.....

Power = W

(2)

(Total 6 marks)

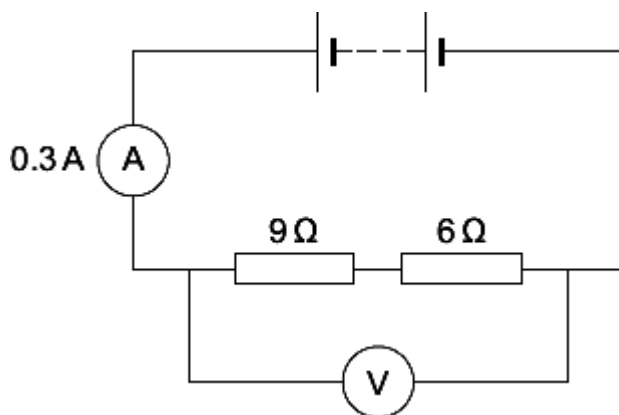Q2. (a) The diagram shows a simple circuit.



(i) Calculate the total resistance of the two resistors in the circuit.

.....

Total resistance = Ω

(1)

(ii) Calculate the reading on the voltmeter.

Show clearly how you work out your answer.

.....

.....

Voltmeter reading = V

(2)

(iii) Draw a ring around the correct answer in the box to complete the sentence.

Replacing one of the resistors with a resistor of higher value will

- | |
|------------|
| decrease |
| not change |
| increase |


the reading on the ammeter.

(1)

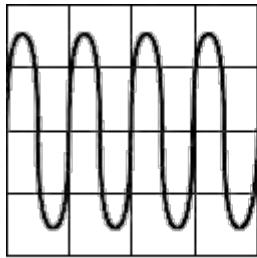
(b) The voltmeter in the circuit is replaced with an oscilloscope.

Which one of the diagrams, **X**, **Y** or **Z**, shows the trace that would be seen on the oscilloscope?


Write your answer, **X**, **Y** or **Z**, in the box.



X

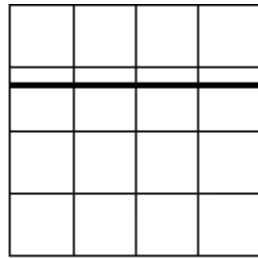

Y

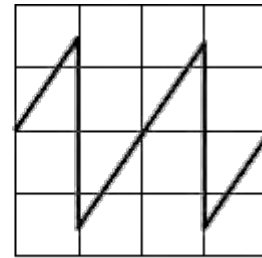

Z

Diagram

Give a reason for your answer.

.....
.....
.....

(2)
(Total 6 marks)

Q3.(a) The diagram shows the information plate on an electric kettle. The kettle is plugged into the a.c. mains electricity supply.

230 V	2760 W
50 Hz	

Use the information from the plate to answer the following questions.

(i) What is the frequency of the a.c. mains electricity supply?

.....

(1)

(ii) What is the power of the electric kettle?

.....

(1)

(b) To boil the water in the kettle, 2400 coulombs of charge pass through the heating element in 200 seconds.

Calculate the current flowing through the heating element and give the unit.

Choose the unit from the list below.

amps

volts


watts

.....
.....
.....

Current =

(3)

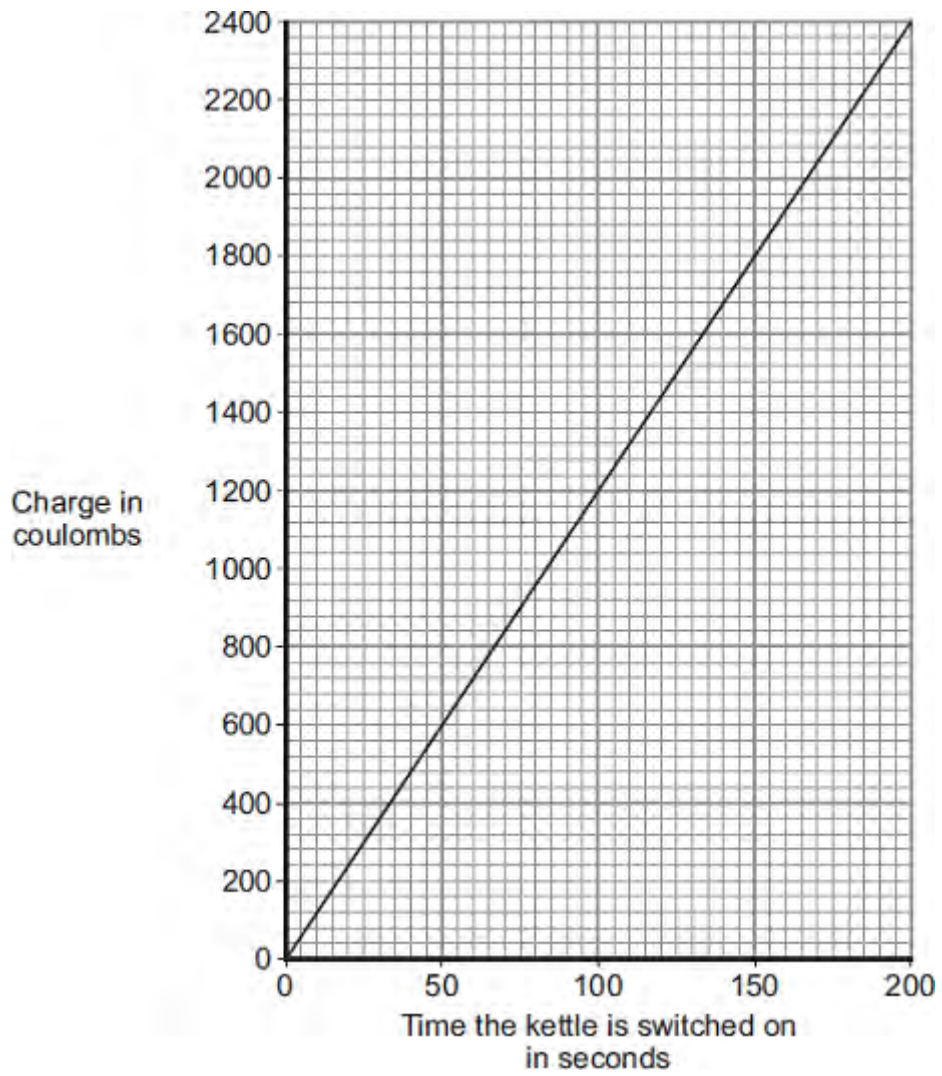(c) The amount of charge passing through the heating element of an electric kettle depends on the time the kettle is switched on.



What pattern links the amount of charge passing through the heating element and the time the kettle is switched on?


.....

.....

(2)
(Total 7 marks)

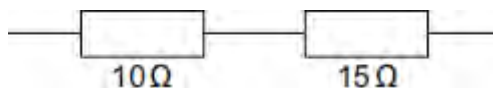Q4.(a) Electrical circuits often contain resistors.

The diagram shows **two** resistors joined in series.




Calculate the total resistance of the **two** resistors.

.....

Total resistance = Ω

(1)

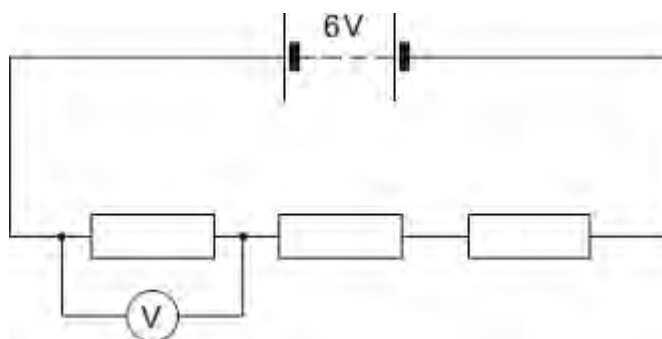(b) A circuit was set up as shown in the diagram. The three resistors are identical.




(i) Calculate the reading on the voltmeter.

.....
.....

Reading on voltmeter = V

(2)

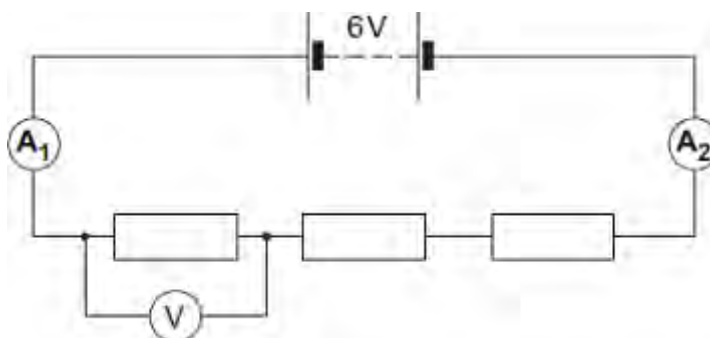(ii) The same circuit has now been set up with two ammeters.



Draw a ring around the correct answer in the box to complete the sentence.


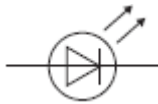
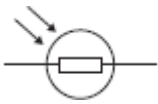
The reading on ammeter A_2 will be

smaller than
equal to
greater than

the reading on ammeter A_1 .

(1)
(Total 4 marks)

Q5.(a) Draw **one** line from each circuit symbol to its correct name.

Circuit symbol	Name
	Diode
	Light-dependent resistor (LDR)
	Lamp
	Light-emitting diode (LED)


(3)

(b) **Figure 1** shows three circuits.

The resistors in the circuits are identical.

Each of the cells has a potential difference of 1.5 volts.

Figure 1

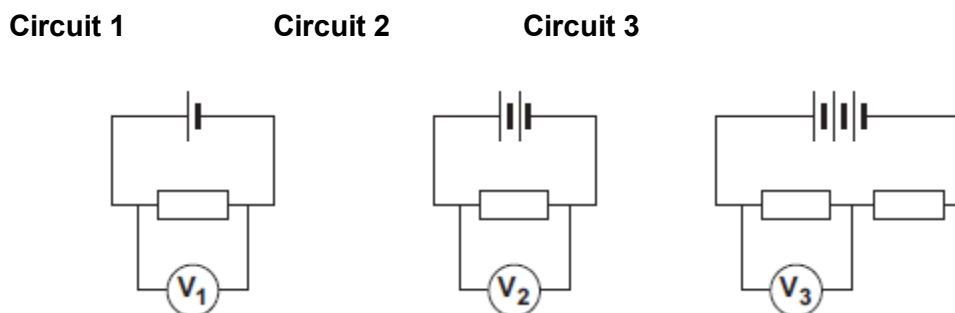

(i) Use the correct answer from the box to complete the sentence.

half	twice	the same as
-------------	--------------	--------------------

The resistance of **circuit 1** is the resistance of **circuit 3**.

(1)

(ii) Calculate the reading on voltmeter V_2 .

.....

Voltmeter reading $V_2 = \dots\dots\dots$ V

(1)

(iii) Which voltmeter, V_1 , V_2 or V_3 , will give the lowest reading?

Draw a ring around the correct answer.

V_1

V_2


V_3

(1)

(c) A student wanted to find out how the number of resistors affects the current in a series circuit.

Figure 2 shows the circuit used by the student.

Figure 2

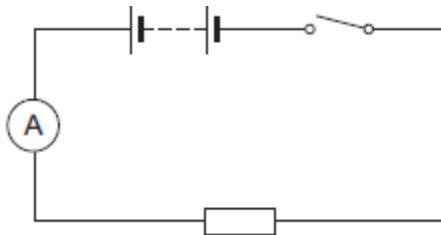


The student started with one resistor and then added more identical resistors to the circuit.

Each time a resistor was added, the student closed the switch and took the ammeter reading.

The student used a total of 4 resistors.

Figure 3 shows three of the results obtained by the student.

Figure 3

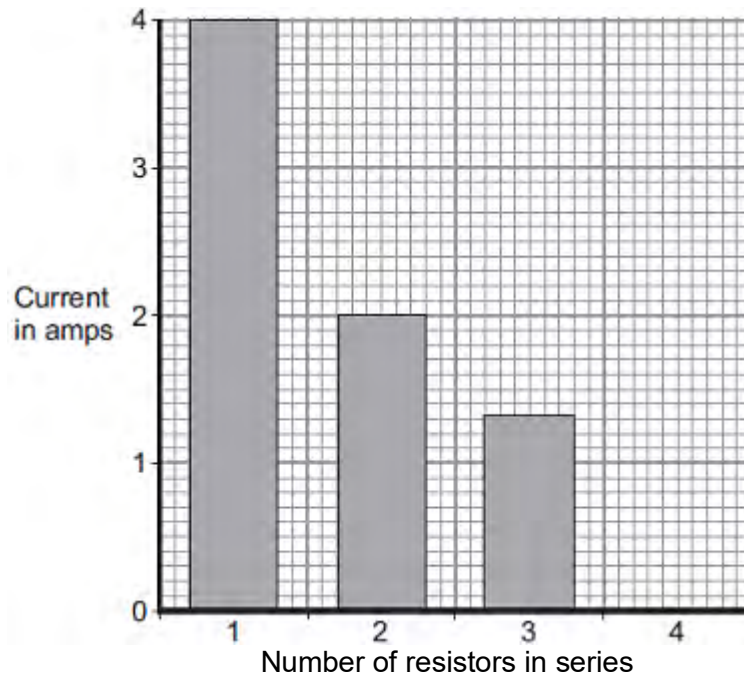

- (i) To get valid results, the student kept one variable the same throughout the experiment.

Which variable did the student keep the same?

.....

(1)

- (ii) The bar chart in **Figure 3** is not complete. The result using 4 resistors is not shown.

Complete the bar chart to show the current in the circuit when 4 resistors were used.

(2)

- (iii) What conclusion should the student make from the bar chart?

.....






.....

(1)

(Total 10 marks)

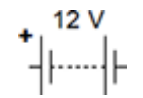Q6.A student wants to investigate how the current through a filament lamp affects its resistance.

(a) Use the circuit symbols in the boxes to draw a circuit diagram that she could use.

12 V battery	variable resistor	filament lamp	voltmeter	ammeter
				

(2)

(b) Describe how the student could use her circuit to investigate how the current through a filament lamp affects its resistance.

.....

.....

.....

.....

.....

.....


.....

.....

(4)

(c) The student's results are shown in **Figure 1**.

Figure 1

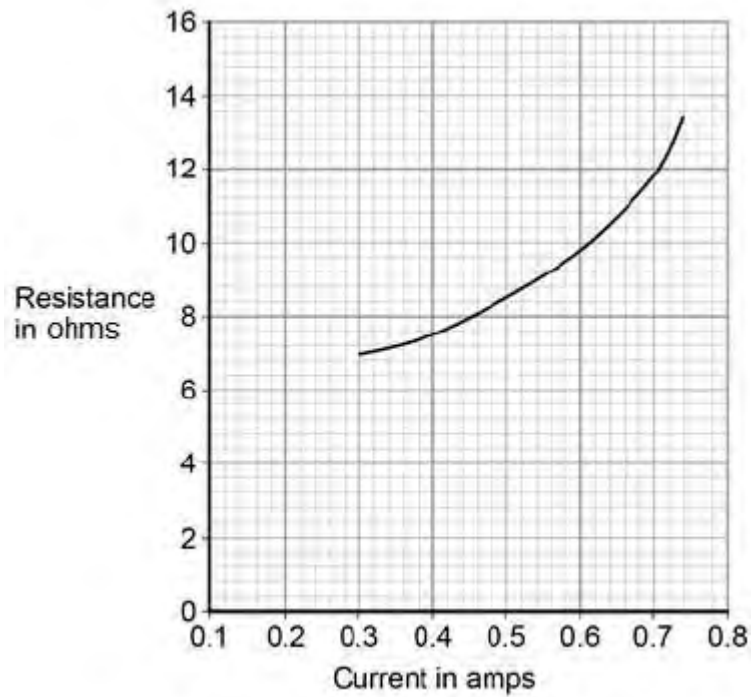

Describe how the resistance of the filament lamp changes as the current through it increases.

.....
.....

(1)

- (d) Use **Figure 1** to estimate the resistance of the filament lamp when a current of 0.10 A passes through the lamp.

Resistance = Ω


(1)

- (e) The current- potential difference graphs of three components are shown in **Figure 2**.


Use answers from the box to identify each component.

diode	filament lamp	light dependent resistor
resistor at constant temperature		thermistor


Figure 2

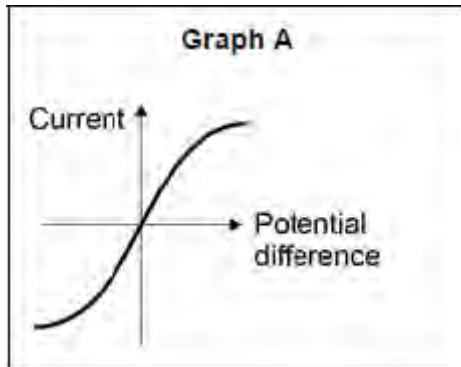

.....

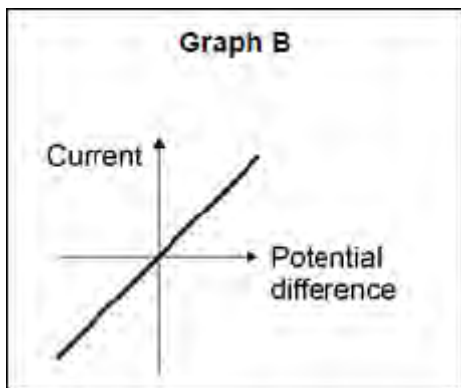


.....

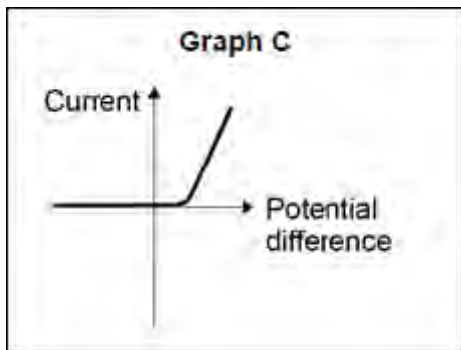

.....

(3)
(Total 11 marks)

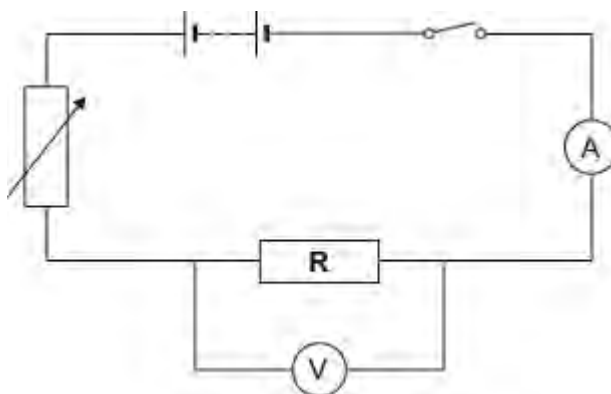Q7.(a) A resistor is a component that is used in an electric circuit.



(i) Describe how a student would use the circuit to take the readings necessary to determine the resistance of resistor **R**.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(6)

(ii) Explain why the student should open the switch after each reading.

.....

.....

.....
.....

(2)

- (iii) In an experiment using this circuit, an ammeter reading was 0.75 A.
The calculated value of the resistance of resistor **R** was 16 Ω .

What is the voltmeter reading?

.....
.....

Voltmeter reading = V

(2)

- (iv) The student told his teacher that the resistance of resistor **R** was 16 Ω .

The teacher explained that the resistors used could only have one of the following values of resistance.

10 Ω 12 Ω 15 Ω 18 Ω 22 Ω

Suggest which of these resistors the student had used in his experiment.

Give a reason for your answer.

.....
.....
.....
.....

(2)

- (b) The diagram shows a fuse.



Describe the action of the fuse in a circuit.

.....

.....

.....

.....

.....

.....

.....

.....

(3)
(Total 15 marks)

M1. (a) $V = 0.10 \times 45$ 1

4.5 (V) 1

(b) $R = 12 / 0.10$ 1

total resistance = 120 (Ω) 1

$R = 120 - 105 = 15$ (Ω) 1

(c) (total) resistance decreases 1

(so) current increases 1

[7]

- M2. (a) (i) also double
increases is insufficient 1
- (ii) variable resistor
accept rheostat / potentiometer 1
- (b) (i) the data / results / variables are continuous
accept data / results / variables are not categoric / discrete 1
- (ii) misreading the ammeter
do not accept misreading the meter / results
do not accept misreading the ammeter and / or voltmeter
reading / human error is insufficient 1
- (iii) straight line from the origin drawn passing close / through
points at 1 V, 5 V, 6 V and ignoring anomalous point
do not accept line drawn 'dot-to-dot' 1
- (iv) yes
mark is for the reason
supports prediction **or** (straight) line passes through the origin
accept a mathematical argument, eg when p.d. went from 2
to 4 the current went from 0.3 to 0.6
it's directly proportional is insufficient 1

[6]

M3. (a) decreases 1

(b) a filament bulb 1
allow bulb

an LED 1

(c) Marks awarded for this answer will be determined by the Quality of Communication (QoC) as well as the standard of the scientific response.

0 marks

No relevant content.

Level 1 (1–2 marks)

There is a basic description of the method. This is incomplete and would not lead to any useful results.

Level 2 (3–4 marks)

There is a description of the method which is almost complete with a few minor omissions and would lead to some results.

Level 3 (5–6 marks)

There is a detailed description of the method which would lead to valid results. To gain full marks an answer including graph, or another appropriate representation of results, must be given.

examples of the physics points made in the response:

- read V and I
- read temperature
- apply heat
- allow hot water to cool*
- read V and I at least one other temperature
- determine R from V / I
- range of temperatures above 50 °C

extra detail:

- use thermometer to read temperature at regular intervals of temperature
- remove source of heat and stir before taking readings
- details of attaining 0 °C or 100 °C
- last reading taken while boiling
- graph of R against T

- at least 3 different temperatures 6

 - (d) (i) Q 1

 - (ii) (80, 3.18) 1

 - (iii) any **one** from:
 - measurement of V too small
 - measurement of I too big
 - incorrect calculation of R
 - thermometer misread

allow misread meter
ignore any references to an error that is systematic


1

 - (iv) any **two** from:
 - not portable
 - *allow requires a lot of equipment allow takes time to set up*
 - needs an electrical supply
 - cannot be read directly

accept it is more difficult to read compared to liquid-in-glass


2
- [14]**

M4. (a) (i) ammeter symbol correct and drawn in series

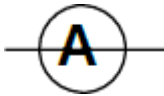
accept
do **not** accept lower case a

1

voltmeter symbol correct and drawn in parallel with the material

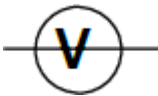
do **not** accept

1

(ii) adjust / use the variable resistor
accept change the resistance

or change the number of cells
accept battery for cell
accept change the pd / accept change the voltage
accept increase / decrease for change

1

(b) (i) 37.5 (Ω)
accept answer between 36 and 39 inclusive

1

(ii) 5.6(25) **or** their (b)(i) \times 0.15
allow 1 mark for correct substitution ie 37.5 **or** their (b)(i) \times 0.15 provided no subsequent step shown

2

(c) (i) the thicker the putty the lower the resistance
answer must be comparative accept the converse

1

(ii) any **one** from:

- measuring length incorrectly
accept may be different length

- measuring current incorrectly
*do **not** accept different currents*
- measuring voltage incorrectly
*do **not** accept different voltage*
- ammeter / voltmeter incorrectly calibrated
- thickness of putty not uniform
*do **not** accept pieces of putty not the same unless qualified*
- meter has a zero error
*do **not** accept systematic / random error*
accept any sensible source of error eg putty at different temperatures
*do **not** accept human error without an explanation*
*do **not** accept amount of putty not same*

1

[8]

M5. (a) (i) to obtain a range of p.d. values
accept increase / decrease current / p.d. / voltage / resistance
accept to change / control the current / p.d. / voltage / resistance
to provide resistance is insufficient
a variable resistor is insufficient
*do **not** accept electricity for current*

1

(ii) temperature of the bulb increases
accept bulb gets hot(ter)
accept answers correctly
expressed in terms of collisions between (free) electrons and ions / atoms
bulb gets brighter is insufficient

1

(iii) 36
allow 1 mark for correct substitution, ie 12×3 provided no subsequent step shown

2

watt(s) / W
accept joules per second / J/s
*do **not** accept w*

1

(b) Marks awarded for this answer will be determined by the Quality of Written Communication (QWC) as well as the standard of the scientific response. Examiners should also refer to the information in the [Marking guidance](#), and apply a 'best-fit' approach to the marking.

0 marksNo relevant content.

Level 1 (1-2 marks)There is a basic comparison of either a cost aspect or an energy efficiency aspect.

Level 2 (3-4 marks)There is a clear comparison of either the cost aspect or

energy efficiency aspect **OR** a basic comparison of both cost and energy efficiency aspects.

Level 3 (5-6 marks) There is a detailed comparison of both the cost aspect and the energy efficiency aspect.

For full marks the comparisons made should support a conclusion as to which type of bulb is preferable.

Examples of the points made in the response:

cost

- halogen are cheaper to buy
simply giving cost figures is insufficient
- 6 halogen lamps cost the same as one LED
- LEDs last longer
- need to buy 18 / more halogen lamps to last the same time as one LED
- 18 halogens cost £35.10
- costs more to run a halogen than LED
- LED has lower maintenance cost (where many used, eg large departmental store lighting)

energy efficiency

- LED works using a smaller current
- LED wastes less energy
- LEDs are more efficient
- LED is 22% more energy efficient
- LED produces less heat
- LED requires smaller input (power) for same output (power)

6
[11]

M6. (a) (i) live 1

(ii) react faster 1

(iii) live and neutral 1

(b) (i) ammeter 1

to measure current
accept to measure amps 1

plus any **one** from:

- variable resistor (1)
to vary current (1)
accept variable power supply
accept change or control
- switch (1)
to stop apparatus getting hot / protect battery
or
to reset equipment (1)
- fuse (1)
to break circuit if current is too big (1)

2


(ii) any **two** from:

- use smaller mass(es)
- move mass closer to pivot
- reduce gap between coil and rocker
- more turns (on coil)*coil / loop*
- iron core in coil
accept use smaller weight(s)

2

[9]

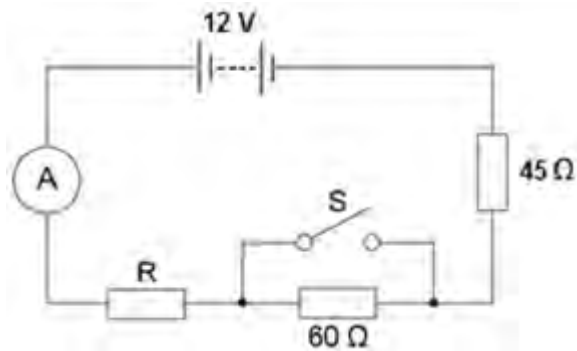Q1. A student set up the electrical circuit shown in the figure below.



(a) The ammeter displays a reading of 0.10 A.

Calculate the potential difference across the 45 Ω resistor.

.....

Potential difference = V

(2)

(b) Calculate the resistance of the resistor labelled **R**.

.....

Resistance = Ω

(3)


(c) State what happens to the total resistance of the circuit and the current through the circuit when switch **S** is closed.

.....

(2)

(Total 7 marks)

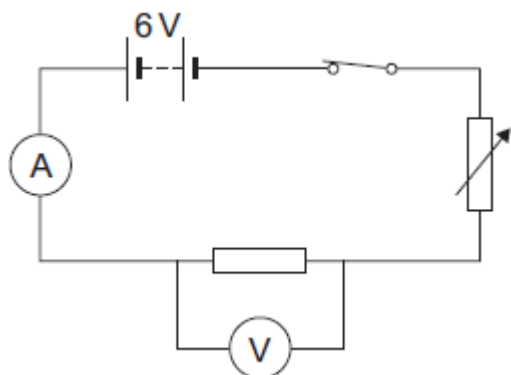Q2. The diagram shows the circuit set up by a student.



(a) The student uses the circuit to test the following hypothesis:

'The current through a resistor is directly proportional to the potential difference across the resistor.'

(i) If the hypothesis is correct, what should the student predict will happen to the current through the resistor when the potential difference across the resistor is doubled?

.....
.....


(1)

(ii) Name the component in the circuit used to change the potential difference across the resistor.

.....

(1)

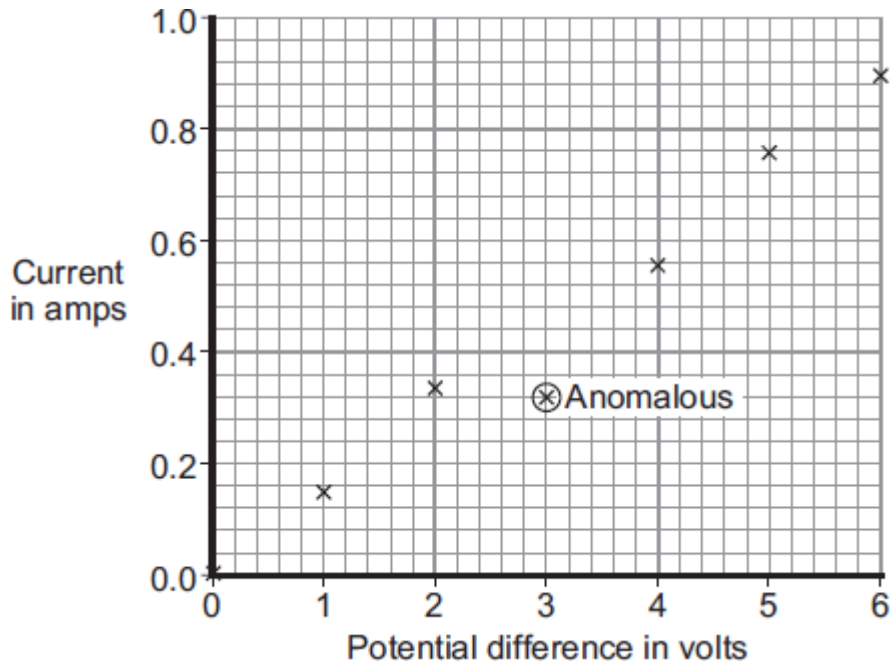(b) The student used the data obtained to plot the points for a graph of current against potential difference.



- (i) Why has the student plotted the points for a line graph and not drawn a bar chart?

.....

(1)

- (ii) One of the points has been identified by the student as being anomalous. What is the most likely cause for this anomalous point?

.....

(1)

- (iii) Draw a line of best fit for these points.

(1)

- (iv) Does the data the student obtained support the hypothesis? Give a reason for your answer.

.....

.....

(1)
(Total 6 marks)

Q3.Electrical circuits have resistance.

- (a) Draw a ring around the correct answer to complete the sentence.

When the resistance of a circuit increases, the current in the circuit

decreases.
increases.
stays the same.

(1)

- (b) Use the correct answer from the box to complete each sentence.

a filament bulb	an LED	an LDR
------------------------	---------------	---------------


An electrical component which has a resistance that increases as the temperature increases is

An electrical component which emits light only when a current flows through it in the forward direction is

(2)

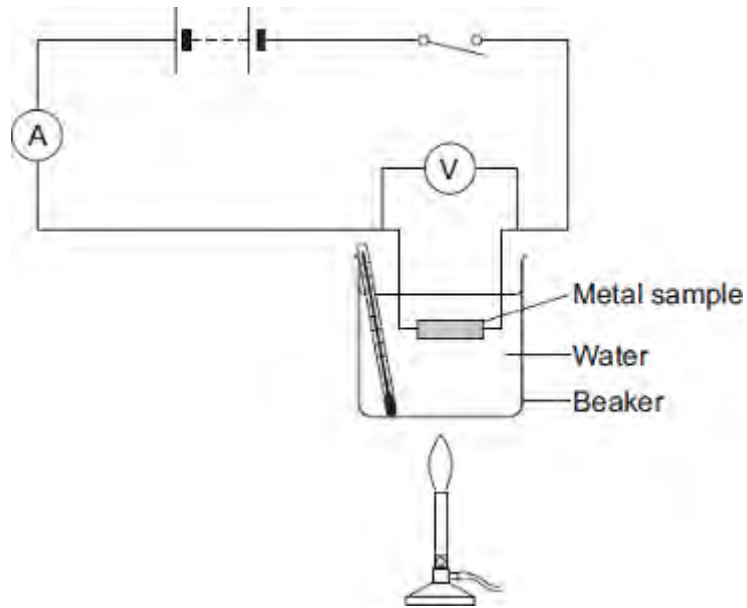- (c) When some metals are heated the resistance of the metal changes.

The equipment for investigating how the resistance of a metal changes when it is heated is shown in the diagram.



In this question you will be assessed on using good English, organising information clearly and using specialist terms where appropriate.

Describe an investigation a student could do to find how the resistance of a metal sample varies with temperature. The student uses the equipment shown.

Include in your answer:

- how the student should use the equipment
- the measurements the student should make
- how the student should use these measurements to determine the resistance
- how to make sure the results are valid.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


(6)

(d) The table shows some data for samples of four metals **P**, **Q**, **R** and **S**.

The metal samples all had the same cross-sectional area and were the same length.

Metal sample	Resistance at 0°C in ohms	Resistance at 100°C in ohms
P	4.05	5.67
Q	2.65	3.48
R	6.0	9.17
S	1.70	2.23

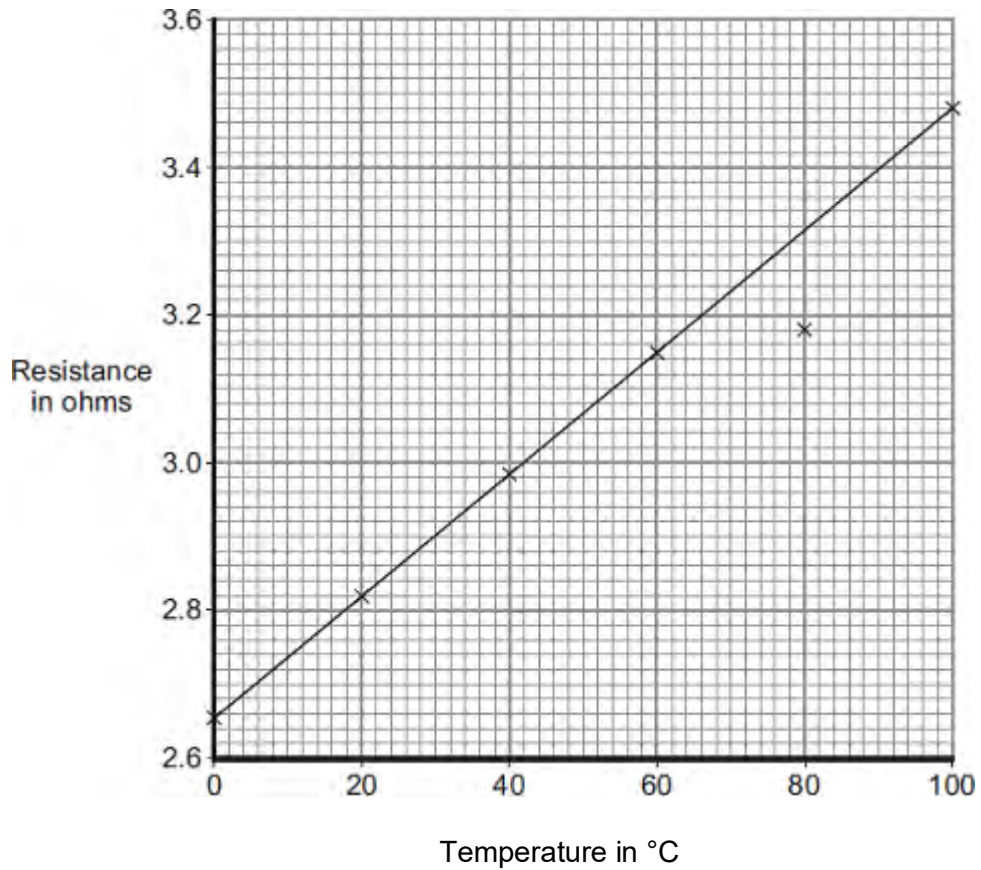A graph of the results for one of the metal samples is shown.



(i) Which metal sample, **P**, **Q**, **R** or **S**, has the data shown in the graph?

(1)

(ii) One of the results is anomalous. Circle this result on the graph.

(1)


(iii) Suggest a reason for the anomalous result.

.....

(1)

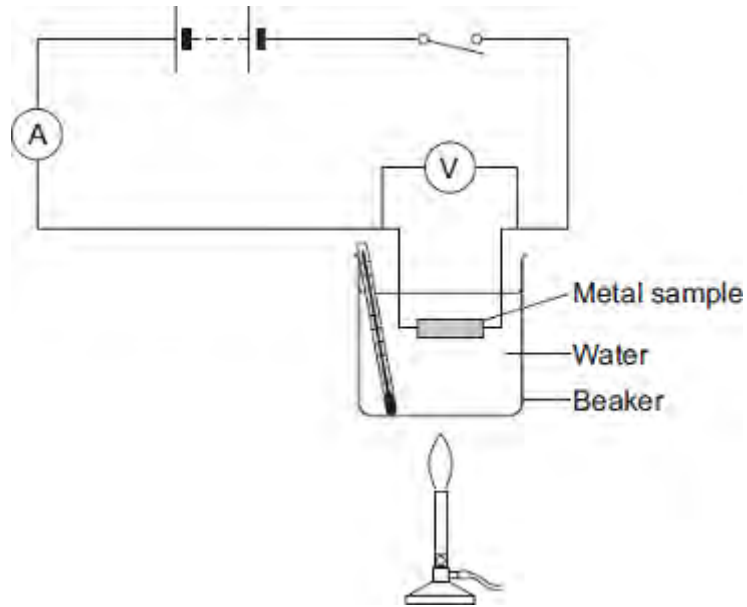(iv) The same equipment used in the investigation could be used as a

thermometer known as a 'resistance thermometer.'




Suggest **two** disadvantages of using this equipment as a thermometer compared to a liquid-in-glass thermometer.

- 1
-
- 2
-

(2)
(Total 14 marks)

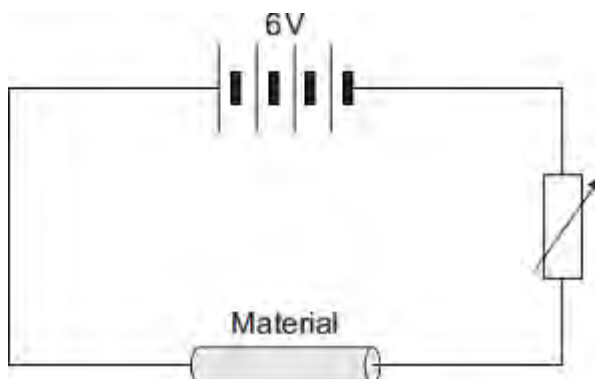- Q4.(a)** The diagram shows the circuit used to investigate the resistance of a sample of a material.
The diagram is not complete; the ammeter and voltmeter are missing.



- (i) Draw the symbols for the ammeter and voltmeter on the diagram in the correct places.

(2)

- (ii) How can the current through the material be changed?


.....
.....

(1)

- (b) The material, called conducting putty, is rolled into cylinders of different lengths but with equal thickness.

Graph 1 shows how the resistance changes with length.

Graph 1

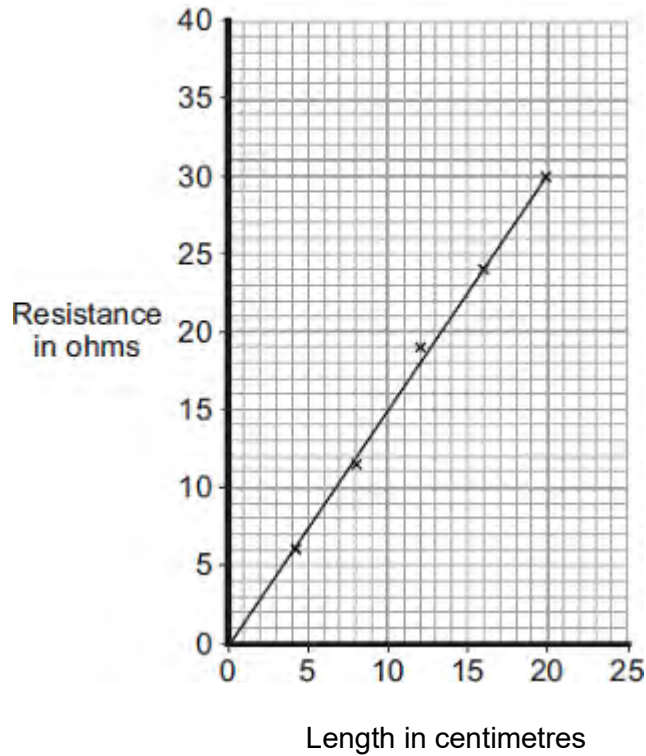

- (i) The current through a 25 cm length of conducting putty was 0.15 A.
Use **Graph 1** to find the resistance of a 25 cm length of conducting putty.

Resistance = ohms

(1)

- (ii) Use your answer to **(b) (i)** to calculate the potential difference across a 25 cm length of conducting putty.

Show clearly how you work out your answer.


.....
.....
.....

Potential difference = volts

(2)

- (c) A second set of data was obtained using thicker pieces of conducting putty. Both sets of results are shown in **Graph 2**.

Graph 2

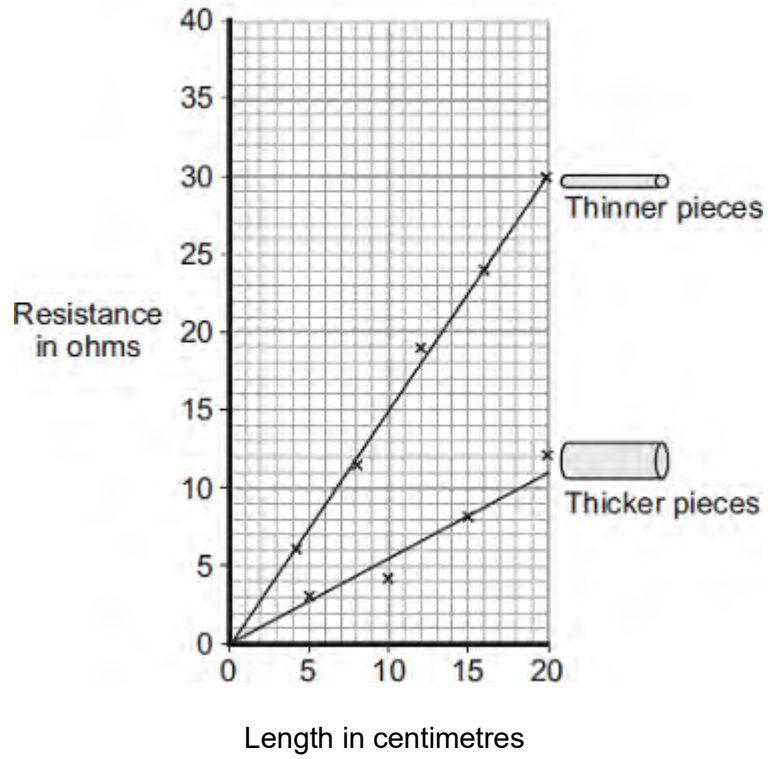

- (i) What is the relationship between the resistance and the thickness of the conducting putty?

.....
.....

(1)


- (ii) Name **one** error that may have reduced the accuracy of the results.

.....

(1)

(Total 8 marks)

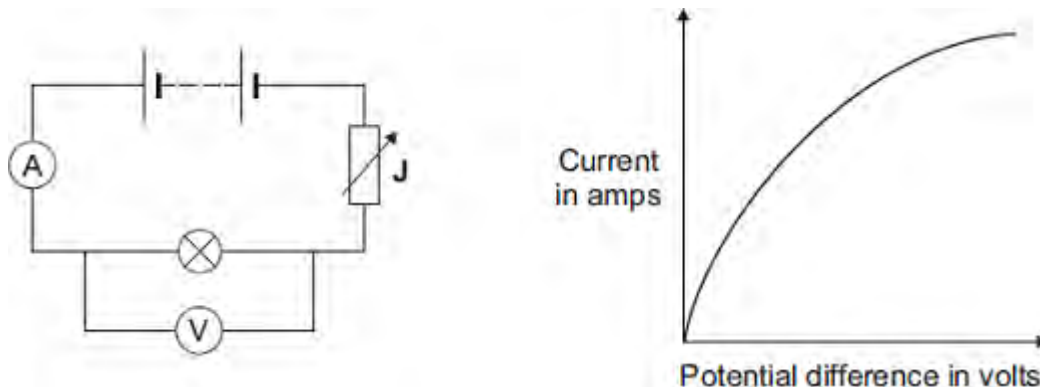Q5.(a) The diagram shows the circuit used to obtain the data needed to plot the current–potential difference graph for a filament bulb.



(i) Why is the component labelled 'J' included in the circuit?

.....

(1)

(ii) The resistance of the bulb increases as the potential difference across the bulb increases. Why?

.....

(1)

(iii) The bulb is at full brightness when the potential difference across the bulb is 12 V.
 The current through the bulb is then 3 A.

Calculate the power of the bulb when it is at full brightness and give the unit.

.....

Power =

(3)

(b) *In this question you will be assessed on using good English, organising information*

clearly and using specialist terms where appropriate.

The table gives data about two types of light bulb people may use in their homes.

Type of light bulb	Energy efficiency	Cost of one light bulb	Average lifetime in hours
Halogen	10%	£1.95	2 000
Light Emitting Diode (LED)	32%	£11.70	36 000

Both types of light bulb produce the same amount of light.

Evaluate, in terms of cost and energy efficiency, the use of the two types of light bulb.

To gain full marks you must compare both types of light bulb and conclude which light bulb would be the best to use.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(6)
(Total 11 marks)

Q6. If a fault develops in an electrical circuit, the current may become too great. The circuit needs to be protected by being disconnected.

A fuse or a circuit breaker may be used to protect the circuit.
One type of circuit breaker is a Residual Current Circuit Breaker (RCCB).

(a) (i) Use the correct answer from the box to complete the sentence.

earth	live	neutral
--------------	-------------	----------------

A fuse is connected in the wire.

(1)

(ii) Use the correct answer from the box to complete the sentence.

are bigger	are cheaper	react faster
-------------------	--------------------	---------------------

RCCBs are sometimes preferred to fuses because they

(1)

(iii) RCCBs operate by detecting a difference in the current between two wires.

Use the correct answer from the box to complete the sentence.

earth and live	earth and neutral	live and neutral
-----------------------	--------------------------	-------------------------


The two wires are the wires.

(1)

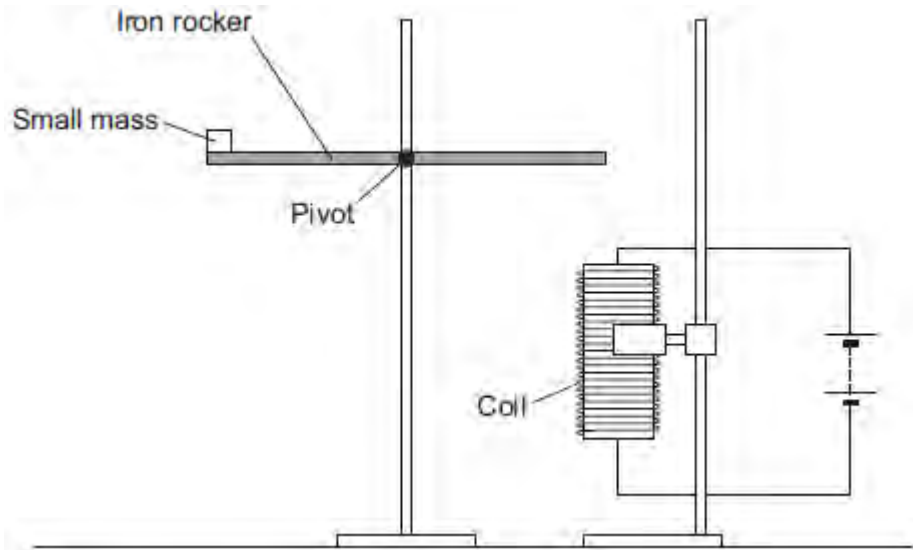(b) An RCCB contains an iron rocker and a coil.

A student investigated how the force of attraction, between a coil and an iron rocker, varies with the current in the coil.

She supported a coil vertically and connected it in an electrical circuit, part of which is shown in the figure below .



She put a small mass on the end of the rocker and increased the current in the coil until the rocker balanced. She repeated the procedure for different masses.

Some of her results are shown in the table below.

Mass in grams	Current needed for the rocker to balance in amps
5	0.5
10	1.0
15	1.5
20	2.0

- (i) State **two** extra components that must have been included in the circuit in the figure above to allow the data in the above table to be collected.

Give reasons for your answers.

.....

.....

.....

.....

.....

.....

.....

.....

(4)

(ii) A teacher said that the values of current were too high to be safe.

Suggest **two** changes that would allow lower values of current to be used in this investigation.

Change 1

.....


Change 2

.....

(2)

(Total 9 marks)

M1.(a)

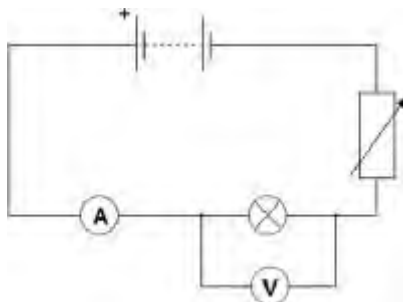

battery in series with bulb and ammeter

1

voltmeter in parallel with bulb

1

variable resistor

or

variable power pack

or

potentiometer

1

(b) A is brighter because it has a higher current (than lamp B at any p.d.)

1

(therefore A has a) higher power output (than bulb B)

accept higher energy output per second

1

(c) lower current (than lamp A) for the same potential difference

accept answer in terms of $R = V / I$

1

lower gradient (than lamp A)

1

(d) 0 – 2 Volts

allow a range from 0 V up to any value between 1 and 2 V.

1

(for an ohmic conductor) current is directly proportional to potential difference

allow lines (of best fit) are straight and pass through the origin


1

(so) resistance is constant

1

[10]

M2. (a) (i)

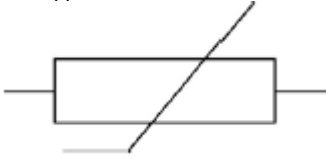


1

(ii) 360

allow 1 mark for correct substitution, ie $9 = 0.025 \times R$

2

(iii) sketch graph of correct shape, ie

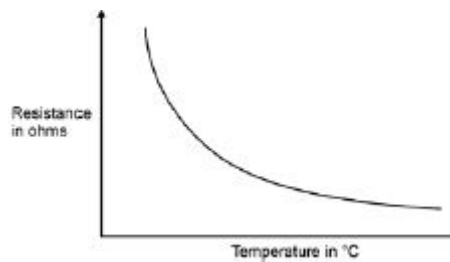

1

(iv) An automatic circuit to switch a heating system on and off.

1

(b) so ammeter reduces / affects current as little as possible
accept so does not reduce / change the current (it is measuring)
accurate reading is insufficient
not change the resistance is insufficient

1

(c) gives a common understanding
accept is easier to share results
accept can compare results
do not need to be converted is insufficient
prevent errors is insufficient

1

- (d) replace Bunsen (and water) with a lamp
accept any way of changing light level

1

replace thermometer with light sensor
accept any way of measuring a change in light level
datalogger alone is insufficient

1

[9]

M3. (a) 35

an answer with more than 2 sig figs that rounds to 35 gains 2 marks

allow 2 marks for correct method, ie $\frac{230}{6.5}$

allow 1 mark for $I = 6.5$ (A) or $R = \frac{230}{26}$

an answer 8.8 gains 2 marks

an answer with more than 2 sig figs that rounds to 8.8 gains 1 mark

3

(b) (maximum) current exceeds maximum safe current for a 2.5 mm² wire
accept power exceeds maximum safe power for a 2.5 mm² wire

*or (maximum) current exceeds 20 (A)
(maximum) current = 26 (A) is insufficient*

1

a 2.5 mm² wire would overheat / melt
*accept socket for wire
do **not** accept plug for wire*

1

(c) a.c. is constantly changing direction
*accept a.c. flows in two directions
accept a.c. changes direction
a.c. travels in different directions is insufficient*

1

d.c. flows in one direction only

1

[7]

M4. (a) attempt to draw four cells in series 1

correct circuit symbols

*circuit symbol should show a long line and a short line,
correctly joined together*

example of correct circuit symbol:



1

(b) (i) 6 (V)
allow 1 mark for correct substitution, ie
 $V = 3 \times 2$ scores 1 mark
provided no subsequent step 2

(ii) 12 (V)
ecf from part (b)(i)
 $18 - 6$
or
 $18 -$ their part (b)(i) scores 1 mark 2

(iii) 9 (Ω)
ecf from part (b)(ii) correctly calculated
 $3 +$ their part (b)(ii) / 2
or
 $18 / 2$ scores 1 mark
provided no subsequent step 2

(c) (i) need a.c. 1

battery is d.c. 1

(ii) 3 (A)

allow 1 mark for correct substitution, ie
 $18 \times 2 = 12 \times I_s$ scores 1 mark

2

[12]


- M5.** (a) (because the) potential of the live wire is 230 V 1
- (and the) potential of the electrician is 0 V 1
- (so there is a) large potential difference between live wire and electrician 1
- charge / current passes through his body
allow voltage for potential difference 1
- (b) diameter between 3.50 and 3.55 (mm)
allow correct use of value of cross-sectional area of 9.5 to 9.9 (mm²) with no final answer given for 1 mark 2
- (c) $18000 = I \times 300$ 1
- $I = 18000 / 300 = 60$ 1
- $13\,800 = (60^2) \times R$ 1
- $R = 13\,800 / 60^2$ 1
- 3.83 (Ω) 1

*allow 3.83(Ω) with no working shown for 5 marks
answer may also be correctly calculated using $P = IV$ and $V = IR$ if 230 V is used.*

[11]

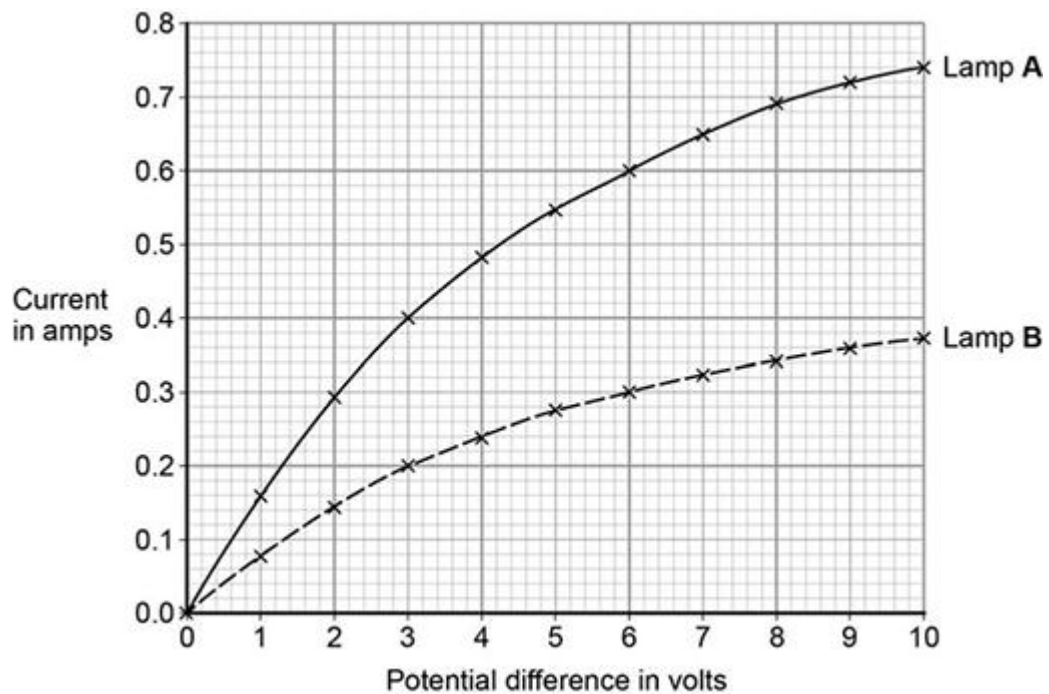Q1. A student investigated how current varies with potential difference for two different lamps.

Her results are shown in the figure below.



- (a) Complete the circuit diagram for the circuit that the student could have used to obtain the results shown in the figure above.



(3)

- (b) Which lamp will be brighter at any potential difference?

Explain your answer.

Use the figure above to aid your explanation

.....

.....

.....

.....

(2)

- (c) Lamp **B** has the higher resistance at any potential difference.

Explain how the figure above shows this.

.....
.....
.....
.....

(2)

- (d) Both lamps behave like ohmic conductors through a range of values of potential difference.

Use the figure above to determine the range for these lamps.

Explain your answer.


.....
.....
.....
.....
.....
.....

(3)

(Total 10 marks)

Q2.(a) **Figure 1** shows the apparatus used to obtain the data needed to calculate the resistance of a thermistor at different temperatures.

Figure 1

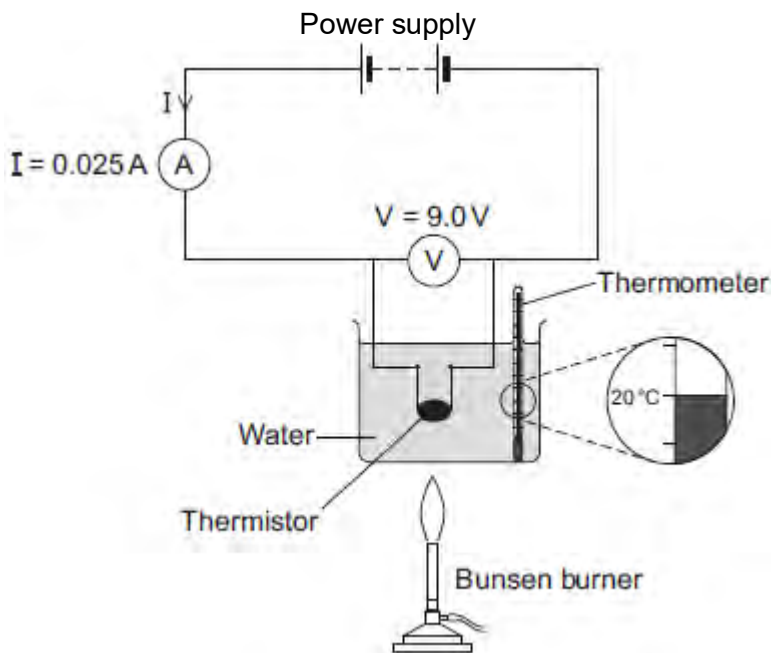

(i) In the box below, draw the circuit symbol for a thermistor.

(1)

(ii) Use the data given in **Figure 1** to calculate the resistance of the thermistor at 20 °C.

.....

.....

.....

Resistance = ohms


(2)

(iii) **Figure 2** shows the axes for a sketch graph.

Complete **Figure 2** to show how the resistance of the thermistor will change

as the temperature of the thermistor increases from 20 °C to 100 °C.

Figure 2

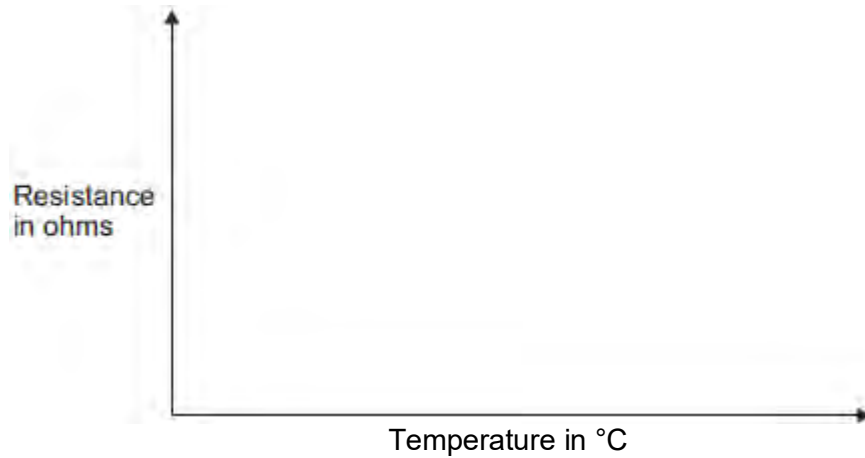

(1)

(iv) Which **one** of the following is most likely to include a thermistor?

Tick (✓) **one** box.

An automatic circuit to switch a plant watering system on and off.

An automatic circuit to switch an outside light on when it gets dark.

An automatic circuit to switch a heating system on and off.

(1)

(b) The ammeter used in the circuit has a very low resistance.

Why is it important that ammeters have a very low resistance?

.....
.....

(1)

(c) The table below gives the temperature of boiling water using three different

temperature scales.

Temperature	Scale
100	Celsius ($^{\circ}\text{C}$)
212	Fahrenheit ($^{\circ}\text{F}$)
80	Réaumur ($^{\circ}\text{Re}$)

Scientists in different countries use the same temperature scale to measure temperature.

Suggest **one** advantage of doing this.

.....
.....
.....

(1)

- (d) A student plans to investigate how the resistance of a light-dependent resistor (LDR) changes with light intensity.

The student starts with the apparatus shown in **Figure 2** but makes three changes to the apparatus.

One of the changes the student makes is to replace the thermistor with an LDR.


Describe what other changes the student should make to the apparatus.

.....
.....
.....
.....

(2)

(Total 9 marks)

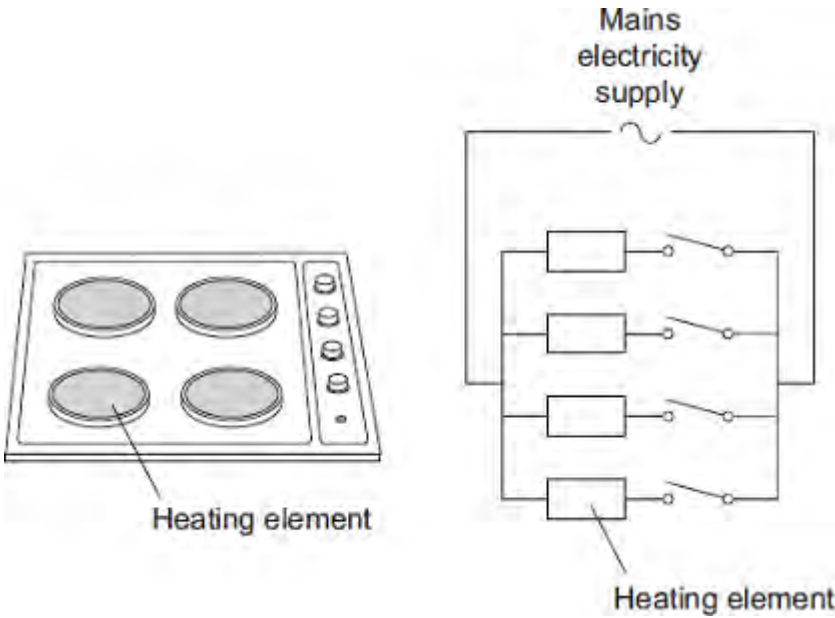Q3. The picture shows an electric cooker hob. The simplified circuit diagram shows how the four heating elements connect to the mains electricity supply. The heating elements are identical.



When all four heating elements are switched on at full power the hob draws a current of 26 A from the 230 V mains electricity supply.

- (a) Calculate the resistance of one heating element when the hob is switched on at full power.

Give your answer to 2 significant figures.

.....

.....

.....

Resistance = Ω

(3)

- (b) The table gives the maximum current that can safely pass through copper wires of different cross-sectional area.

Cross-sectional area in mm ²	Maximum safe current in amps
1.0	11.5
2.5	20.0

4.0	27.0
6.0	34.0

The power sockets in a home are wired to the mains electricity supply using cables containing 2.5 mm^2 copper wires. Most electrical appliances are connected to the mains electricity supply by plugging them into a standard power socket.

It would **not** be safe to connect the electric cooker hob to the mains electricity supply by plugging it into a standard power socket.

Why?

.....

.....

.....

.....

(2)

- (c) Mains electricity is an alternating current supply. Batteries supply a direct current.

What is the difference between an alternating current and a direct current?

.....

.....

.....

.....

(2)

(Total 7 marks)

Q4. The current in a circuit depends on the potential difference (p.d.) provided by the cells and the total resistance of the circuit.

- (a) Using the correct circuit symbols, draw a diagram to show how you would connect 1.5 V cells together to give a p.d. of 6 V.


(2)

- (b) **Figure 1** shows a circuit containing an 18 V battery.

Two resistors, **X** and **Y**, are connected in series.

- **X** has a resistance of 3Ω .
- There is a current of 2 A in **X**.

Figure 1

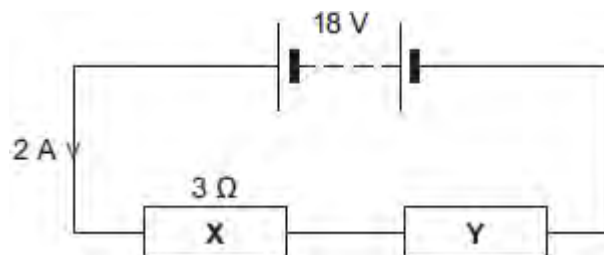

- (i) Calculate the p.d. across **X**.

.....

P.d. across **X** = V

(2)

- (ii) Calculate the p.d. across **Y**.

.....

P.d. across **Y** = V

(2)

(iii) Calculate the total resistance of X and Y.


.....
.....
.....

Total resistance of X and Y = Ω

(2)

(c) **Figure 2** shows a transformer.

Figure 2

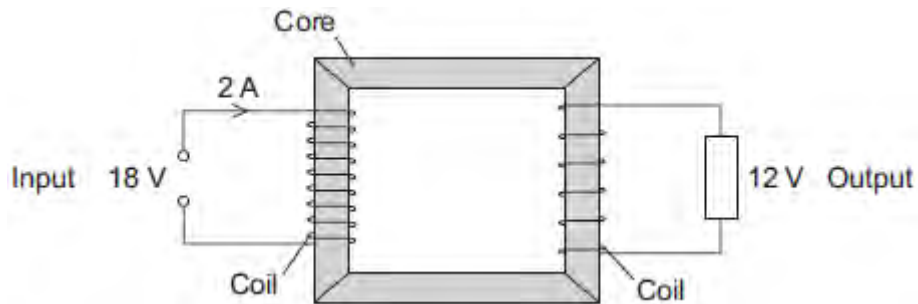

(i) An 18 V battery could **not** be used as the input of a transformer.

Explain why.

.....
.....
.....
.....

(2)

(ii) The transformer is 100% efficient.

Calculate the output current for the transformer shown in **Figure 2**.

.....
.....
.....

Output current = A

(2)
(Total 12 marks)

Q5.An electrician is replacing an old electric shower with a new one.

The inside of the old shower is shown in **Figure 1**.

Figure 1



© Michael Priest

(a) If the electrician touches the live wire he will receive an electric shock.

Explain why.

.....

.....

.....

.....

.....

.....

.....

.....


.....

(4)

- (b) Different electrical wires need to have a cross-sectional area that is suitable for the power output.

Figure 2 shows the recommended maximum power input to wires of different cross-sectional areas.

Figure 2

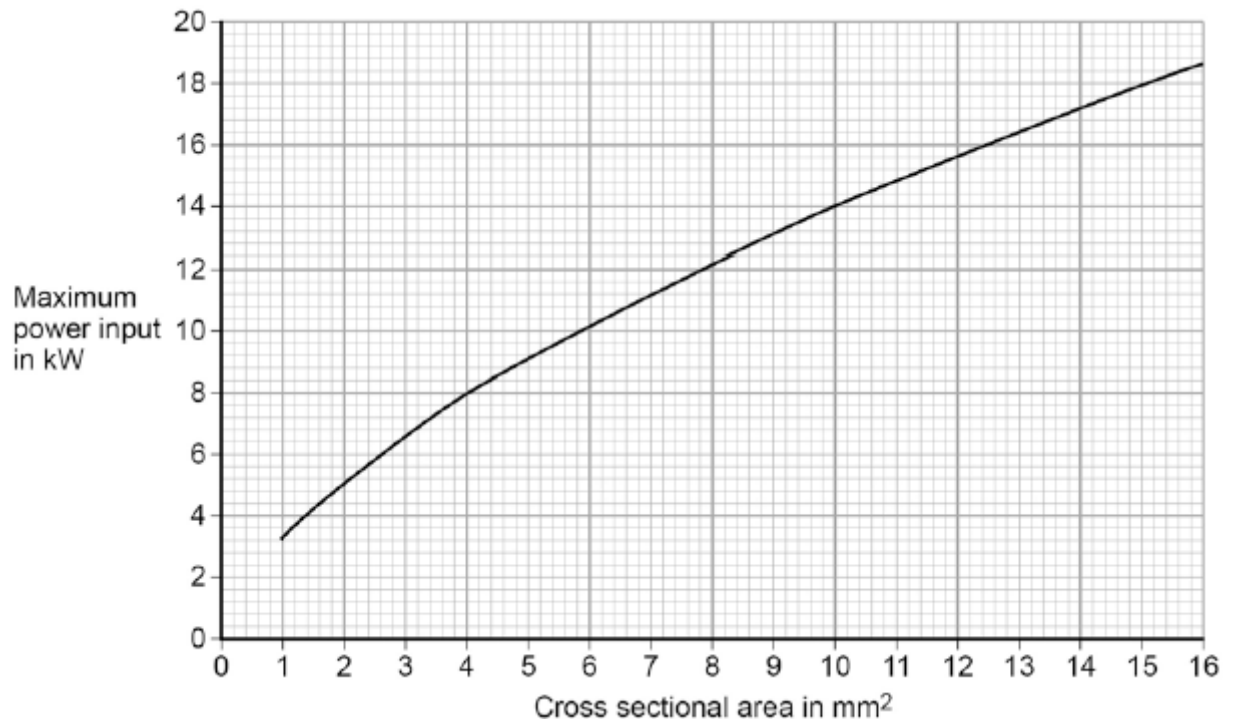

The new electric shower has a power input of 13.8 kW.

Determine the minimum **diameter** of wire that should be used for the new shower.

The diameter, d , can be calculated using the equation:

$$d = \sqrt{\frac{4A}{\pi}}$$

A is the cross-sectional area of the wire.

.....

Minimum diameter = mm

(2)

- (c) The charge that flows through the new shower in 300 seconds is 18 000 C.

The new electric shower has a power of 13.8 kW.

Calculate the resistance of the heating element in the new shower.

Write down any equations you use.

.....
.....
.....
.....
.....
.....
.....
.....

Resistance = Ω

(5)
(Total 11 marks)

- M1.**
- (a) any **two** from:
- nuclear
 - oil
 - (natural) gas
- (b) 4 (hours)
- (c) a system of cables and transformers
- (d) The power output of wind turbines is unpredictable
- (e) $1500 / 0.6$
- 2500 (wind turbines)
- allow 2500 with no working shown for 2 marks*
- (f) Most energy resources have negative environmental effects.

2

1

1

1

1

1

1

[8]

- M2. (a) iron 1
- hairdryer 1
- kettle 1
- answers can be in any order*
- (b) (i) Y 1
- (ii) bar drawn with any height greater than Y
ignore width of bar 1
- (c) (bigger volume) takes more time (to boil)
accept explanation using data from graph 1
- (so) more energy transferred
do not accept electricity for energy 1
- (and) this costs more money
ignore reference to cost of water
wasting more money because heating more water than
needed is insufficient 1

[8]

- M3.(a)** *there is a magnetic field (around the magnet)* 1
- (this magnetic field) changes / moves* 1
- and cuts through coil*
accept links with coil 1
- so a p.d. induced across coil* 1
- the coil forms a complete circuit* 1
- so a current (is induced)* 1
- (b) *ammeter reading does not change*
must be in this order
accept ammeter has a small reading / shows a current 1
- zero* 1
- greater than before*
accept a large(r) reading 1
- same as originally but in the opposite direction*
accept a small reading in the opposite direction

1

(c) 0.30

allow 1 mark for correct substitution, ie $0.05 = Q / 6$

2

C / coulomb

allow A s

1

[13]

M4.(a) (i) any **six** from:

- switch on
- read both ammeter and voltmeter
allow read the meters
- adjust variable resistor to change the current
- take further readings
- draw graph
- (of) V against I
allow take mean
- $R = V / I$
allow take the gradient of the graph

6

(ii) resistor would get hot if current left on

1

so its resistance would increase

1

(iii) 12 (V)

0.75 × 16 gains 1 mark

2

(iv) 15 (Ω)

1

16 is nearer to that value than any other

1

(b) if current is above 5 A / value of fuse

1

fuse melts

allow blows / breaks

*do **not** accept exploded*

1

breaks circuit

1
[15]

M5. (a) he may receive an electric shock

or

he may be electrocuted

1

if he touches the live wire

1

(b) $10\,690 = I \times 230$

1

$I = 10\,690 / 230$

1

46.478(260) (A)

1

46

1

allow 46 (A) with no working shown for 4 marks

(c) cost is higher

1

more energy is used (per second)

1

[8]

M6.(a) current that is always in the same direction 1

(b) total resistance = 30 (Ω) 1

$$V = 0.4 \times 30$$
1

12 (V) 1

*allow 12 (V) with no working shown for 3 marks
an answer of 8 (V) or 4 (V) gains 2 marks only*

(c) $P = 0.4 \times 12 = 4.8$ 1

5 (W) 1

*allow 5 (W) with no working shown for 2 marks
allow 4.8 (W) with no working shown for 1 mark*

[6]

Q1.Energy resources can be renewable or non-renewable.

(a) Coal is a non-renewable energy resource.

Name **two** other non-renewable energy resources.


1

2

(2)

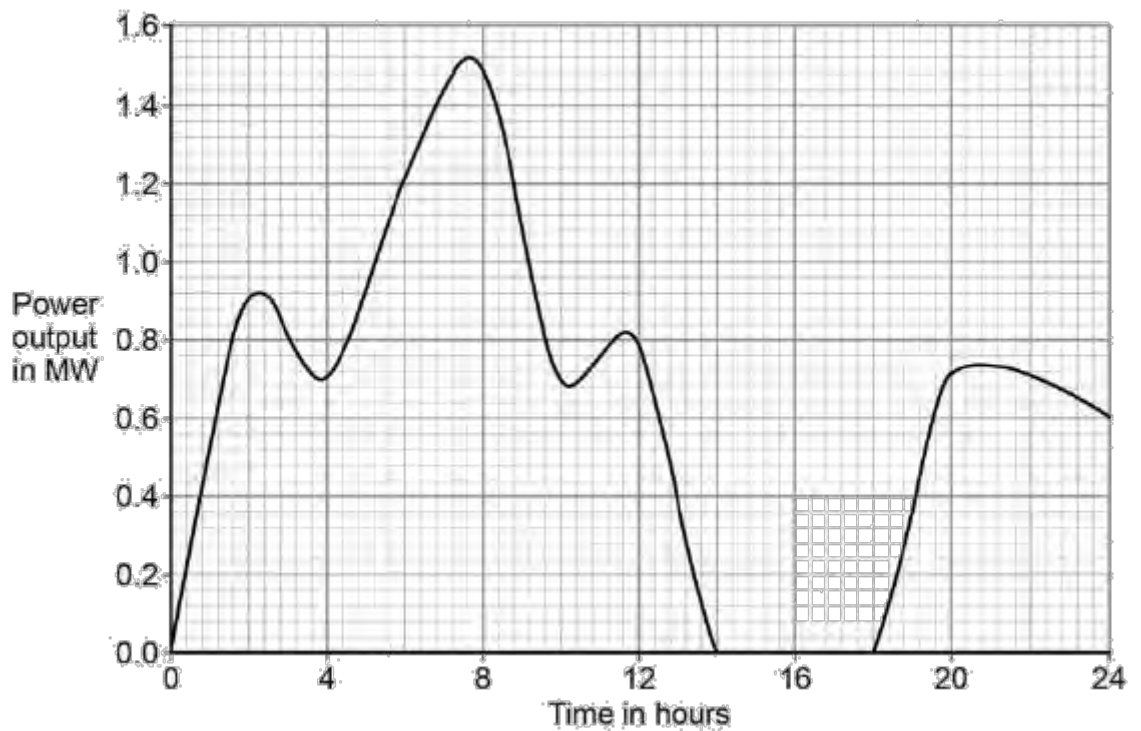(b) Wind turbines are used to generate electricity.

The graph below shows how the power output of a wind turbine changes over one day.



A wind turbine does not generate electricity constantly.

For how many hours did the wind turbine generate no electricity?

.....

Time = hours

(1)

- (c) Electrical power is transferred from power stations to the National Grid.

What is the National Grid?

Tick **one** box.

a system of cables and pylons

a system of cables and transformers

a system of cables, transformers and power stations

(1)

- (d) An island has a large number of wind turbines and a coal-fired power station.

The island needs to use the electricity generated by the coal-fired power station at certain times.

Choose **one** reason why.

Tick **one** box.

Wind is a renewable energy resource.

Wind turbine power output is constant.

The power output of wind turbines is unpredictable.

The fuel cost for wind turbines is very high.

(1)

- (e) A wind turbine has an average power output of 0.60 MW.

A coal-fired power station has a continuous power output of 1500 MW.

Calculate how many wind turbines would be needed to generate the same power output as one coal-fired power station.

.....
.....

Number of wind turbines =

(2)

(f) It is important that scientists develop new energy resources.

Choose **one** reason why.

Tick **one** box.


All energy resources are running out.

All energy resources are used to generate electricity.

Most energy resources have negative environmental effects.

(1)
(Total 8 marks)

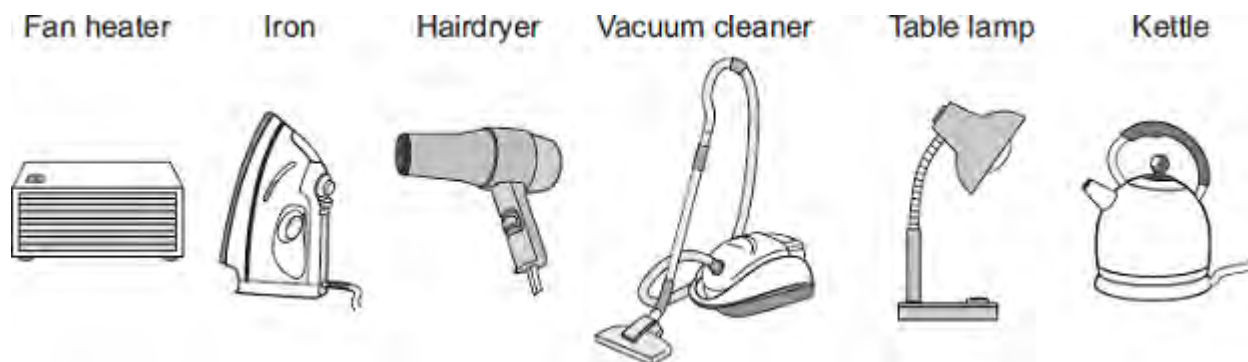Q2. The pictures show six different household appliances.




(a) Four of the appliances, including the fan heater, are designed to transform electrical energy into heat.

Name the other **three** appliances designed to transform electrical energy into heat.

- 1
- 2
- 3

(3)

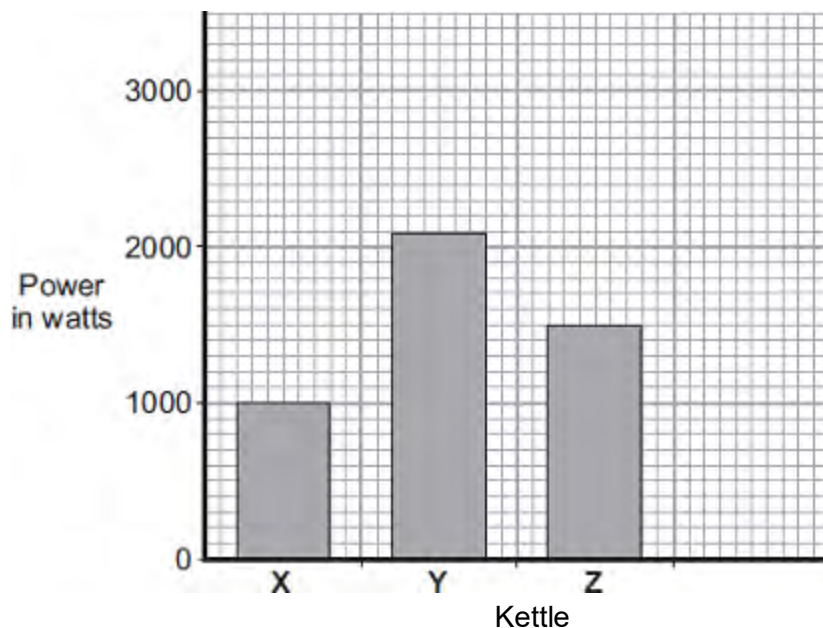(b) The bar chart shows the power of three electric kettles, **X**, **Y** and **Z**.



(i) In one week, each kettle is used for a total of 30 minutes.

Which kettle costs the most to use?

Put a tick (✓) next to your answer.

X

Y

Y


(1)

(ii) A new 'express boil' kettle boils water faster than any other kettle.

Draw a fourth bar on the chart to show the possible power of an 'express boil' kettle.

(1)

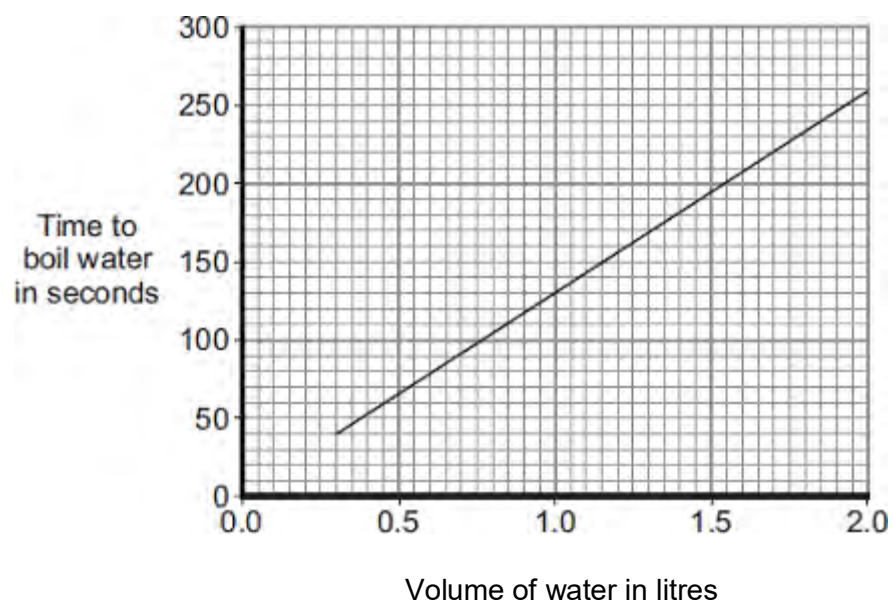(c) The graph shows how the time to boil water in an electric kettle depends on the volume of water in the kettle.



A householder always fills the electric kettle to the top, even when only enough

boiling water for one small cup of coffee is wanted.

Explain how the householder is wasting money.

.....

.....

.....


.....

.....

.....

(3)
(Total 8 marks)

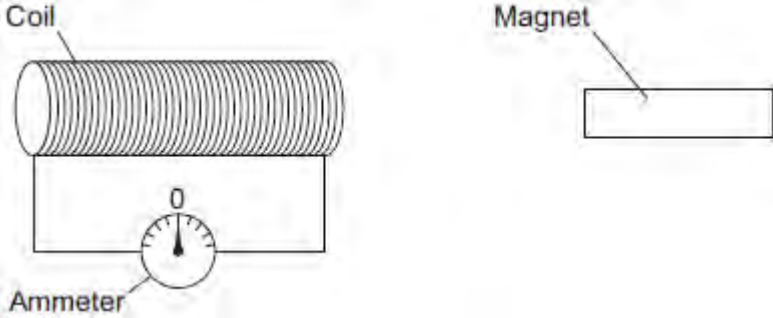Q3. The figure below shows a coil and a magnet. An ammeter is connected to the coil.



The ammeter has a centre zero scale, so that values of current going in either direction through the coil can be measured.

- (a) A teacher moves the magnet slowly towards the coil.

Explain why there is a reading on the ammeter.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(6)

- (b) The table below shows some other actions taken by the teacher.

Complete the table to show the effect of each action on the ammeter reading.

Action taken by teacher	What happens to the ammeter reading?
Holds the magnet stationary and moves the coil slowly towards the magnet	
Holds the magnet stationary within the coil	
Moves the magnet quickly towards the coil	
Reverses the magnet and moves it slowly towards the coil	

(4)

- (c) The magnet moves so that there is a steady reading of 0.05 A on the ammeter for 6 seconds.

Calculate the charge that flows through the coil during the 6 seconds.

Give the unit.

.....


.....

.....

Charge =

(3)
(Total 13 marks)

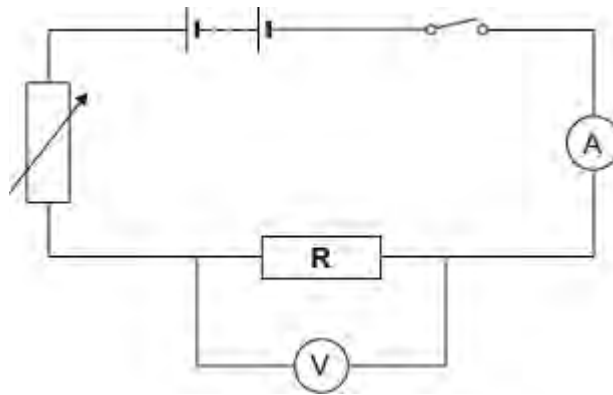Q4.(a) A resistor is a component that is used in an electric circuit.



(i) Describe how a student would use the circuit to take the readings necessary to determine the resistance of resistor **R**.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(6)

(ii) Explain why the student should open the switch after each reading.

.....

.....

.....
.....

(2)

- (iii) In an experiment using this circuit, an ammeter reading was 0.75 A.
The calculated value of the resistance of resistor **R** was 16 Ω .

What is the voltmeter reading?

.....
.....

Voltmeter reading = V

(2)

- (iv) The student told his teacher that the resistance of resistor **R** was 16 Ω .

The teacher explained that the resistors used could only have one of the following values of resistance.

10 Ω 12 Ω 15 Ω 18 Ω 22 Ω

Suggest which of these resistors the student had used in his experiment.

Give a reason for your answer.

.....
.....
.....
.....

(2)

- (b) The diagram shows a fuse.



Describe the action of the fuse in a circuit.

.....

.....

.....

.....

.....

.....

.....

.....

.....

(3)
(Total 15 marks)

Q5.An electrician is replacing an old electric shower with a new one.

The inside of the old shower is shown in the figure below.



© Michael Priest

- (a) The electrician should **not** change the shower unless he switches off the mains electricity supply.

Explain why.

.....

.....

.....

.....

(2)

- (b) The new shower has a power output of 10 690 W when it is connected to the 230 V mains electricity supply.

The equation which links current, potential difference and power is:

$$\text{current} = \frac{\text{power}}{\text{potential difference}}$$

Calculate the current passing through the new shower.

Give your answer to two significant figures.

.....
.....
.....

Current = A

(4)

(c) The new shower has a higher power rating than the old shower.

How does the power of the new shower affect the cost of using the shower?


Give a reason for your answer.

.....
.....
.....
.....

(2)

(Total 8 marks)

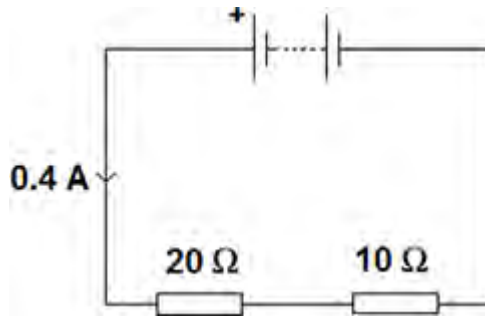Q6. An electrical circuit is shown in the figure below.



(a) The current in the circuit is direct current.

What is meant by direct current?

Tick **one** box.

Current that continuously changes direction.

Current that travels directly to the component.

Current that is always in the same direction.

(1)

(b) The equation which links current, potential difference and resistance is:

$$\text{potential difference} = \text{current} \times \text{resistance}$$

Calculate the potential difference across the battery in the circuit in the figure above.

.....
.....

$$\text{Potential difference} = \dots\dots\dots \text{ V}$$

(3)

(c) The equation which links current, potential difference and power is:

$$\text{power} = \text{current} \times \text{potential difference}$$

Calculate the power output of the battery in the figure above.

Give your answer to one significant figure.

.....

Power = W

(2)

(Total 6 marks)

- M1. (a) (i)** 150 1
- (ii) transferred to the surroundings by heating
reference to sound negates mark 1
- (iii) 0.75
450 / 600 gains 1 mark
accept 75% for 2 marks
maximum of 1 mark awarded if a unit is given 2
- (iv) 20 (s)
correct answer with or without working gains 2 marks
correct substitution of 600 / 30 gains 1 mark 2
- (b) (i) to avoid bias 1
- (ii) use less power and last longer 1
- 1 LED costs £16, 40 filament bulbs cost £80
- or**
- filament costs (5 times) more in energy consumption 1
- (iii) any **one** from:
- availability of bulbs

- colour output
- temperature of bulb surface

1
[10]

M2. (a) brown 1

(b) outside / case is plastic / an insulator
accept is double insulated
accept non-conductor for plastic
do not accept it / hairdryer is plastic 1

(c) (i) (1) S_1
and no other 1

(2) S_1 and S_3
both required, either order 1

(ii) S_1 must be ON (for either heater to work)
do not accept reference to 'fan' switch 1

S_1 switches the fan on 1

(d) 1495
allow 1 mark for correct substitution
ie, 6.5×230 2

watt(s) or W
an answer of 1.495 kW gains 3 marks
although the unit is an independent mark for full credit
the unit and numerical value must be consistent
accept joules per second or J/s 1

[9]

M3. (a) (i) to obtain a range of p.d. values
accept increase / decrease current / p.d. / voltage / resistance
accept to change / control the current / p.d. / voltage / resistance
to provide resistance is insufficient
a variable resistor is insufficient
*do **not** accept electricity for current*

1

(ii) temperature of the bulb increases
accept bulb gets hot(ter)
accept answers correctly
expressed in terms of collisions between (free) electrons and ions / atoms
bulb gets brighter is insufficient

1

(iii) 36
allow 1 mark for correct substitution, ie 12×3 provided no subsequent step shown

2

watt(s) / W
accept joules per second / J/s
*do **not** accept w*

1

(b) Marks awarded for this answer will be determined by the Quality of Written Communication (QWC) as well as the standard of the scientific response. Examiners should also refer to the information in the [Marking guidance](#), and apply a 'best-fit' approach to the marking.

0 marksNo relevant content.

Level 1 (1-2 marks)There is a basic comparison of either a cost aspect or an energy efficiency aspect.

Level 2 (3-4 marks) There is a clear comparison of either the cost aspect or energy efficiency aspect **OR** a basic comparison of both cost and energy efficiency aspects.

Level 3 (5-6 marks) There is a detailed comparison of both the cost aspect and the energy efficiency aspect.

For full marks the comparisons made should support a conclusion as to which type of bulb is preferable.

Examples of the points made in the response:

cost

- halogen are cheaper to buy
simply giving cost figures is insufficient
- 6 halogen lamps cost the same as one LED
- LEDs last longer
- need to buy 18 / more halogen lamps to last the same time as one LED
- 18 halogens cost £35.10
- costs more to run a halogen than LED
- LED has lower maintenance cost (where many used, eg large departmental store lighting)

energy efficiency

- LED works using a smaller current
- LED wastes less energy
- LEDs are more efficient
- LED is 22% more energy efficient
- LED produces less heat
- LED requires smaller input (power) for same output (power)

M4. (a) (i) live 1

(ii) react faster 1

(iii) live and neutral 1

(b) (i) ammeter 1

to measure current
accept to measure amps 1

plus any **one** from:

- variable resistor (1)
to vary current (1)
accept variable power supply
accept change or control
- switch (1)
to stop apparatus getting hot / protect battery
or
to reset equipment (1)
- fuse (1)
to break circuit if current is too big (1)

2

(ii) any **two** from:

- use smaller mass(es)
- move mass closer to pivot
- reduce gap between coil and rocker
- more turns (on coil)*coil / loop*
- iron core in coil

accept use smaller weight(s)

2

[9]

- M5.** (a) (black) is a good absorber of (infrared) radiation 1
- (b) (i) amount of energy required to change (the state of a substance) from solid to liquid (with no change in temperature)
melt is insufficient 1
- unit mass / 1kg 1
- (ii) 5.1×10^6 (J)
accept 5×10^6
allow 1 mark for correct substitution ie $E = 15 \times 3.4 \times 10^5$ 2
- (c) (i) mass of ice
allow volume / weight / amount / quantity of ice 1
- (ii) to distribute the salt throughout the ice 1
- to keep all the ice at the same temperature 1
- (iii) melting point decreases as the mass of salt is increased
allow concentration for mass
accept negative correlation
*do **not** accept inversely proportional* 1
- (d) 60 000 (J)
accept 60 KJ
allow 2 marks for correct substitution ie $E = 500 \times 2.0 \times 60$

allow 2 marks for an answer of 1000 or 60
allow 1 mark for correct substitution ie
 $E = 500 \times 2.0$ or $0.50 \times 2.0 \times 60$
allow 1 mark for an answer of 1

3

- (e) Marks awarded for this answer will be determined by the Quality of Communication (QC) as well as the standard of the scientific response. Examiners should also apply a 'best-fit' approach to the marking.

0 marks

No relevant content

Level 1 (1–2 marks)

There is *an attempt at a description of some advantages or disadvantages.*

Level 2 (3–4 marks)

There is a *basic description of some advantages and / or disadvantages for some of the methods*

Level 3 (5–6 marks)

There is a clear description of the advantages and disadvantages of all the methods.

examples of the points made in the response

extra information

energy storage

advantages:

- no fuel costs
- no environmental effects

disadvantages:

- expensive to set up and maintain
- need to dig deep under road
- dependent on (summer) weather
- digging up earth and disrupting habitats

salt spreading

advantages:

- easily available
- cheap

disadvantages:

- can damage trees / plants / drinking water / cars
- needs to be cleaned away

undersoil heating

advantages:

- not dependent on weather
- can be switched on and off

disadvantages:

- costly
- bad for environment

⁶
[18]

Q1.A student finds some information about energy-saving light bulbs.

(a) A 30W light bulb uses 600J of electrical energy in a certain period of time. In that time, it produces 450 J of light energy. The rest of the energy is wasted.

(i) Calculate the energy wasted by the light bulb in this period of time.

.....

Wasted energy = J

(1)

(ii) What happens to the energy wasted by the light bulb?

.....

.....

(1)

(iii) Calculate the efficiency of this light bulb.

.....

.....

Efficiency =

(2)

(iv) Calculate the period of time, in seconds, during which the 600 J is provided to the 30 W light bulb.

.....

.....

Time = s

(2)

(b) A company that makes light bulbs provides information about some of their products.

The table shows some of this information.

	Power in watts	Lifetime in hours	Cost of bulb in £
Filament bulb	60	1250	2.00
LED bulb	12	50 000	16.00

- (i) Suggest why it is important to confirm this information independently.

.....

(1)

- (ii) A homeowner is thinking about replacing his filament bulbs with LED bulbs.

A 12 W LED bulb gives the same light output as a 60 W filament bulb.

Suggest reasons why the homeowner is likely to choose LED bulbs.

Use the information given in the table.

.....

.....

.....

.....

(2)

- (iii) State **one** factor, other than efficiency, that is important when considering the choice of a bulb for lighting in the home.

.....

.....

(1)

(Total 10 marks)

Q2. Diagram 1 shows a hairdryer.

Diagram 2 shows how the heaters and fan of the hairdryer are connected to a 3-pin plug. The hairdryer does not have an earth wire.

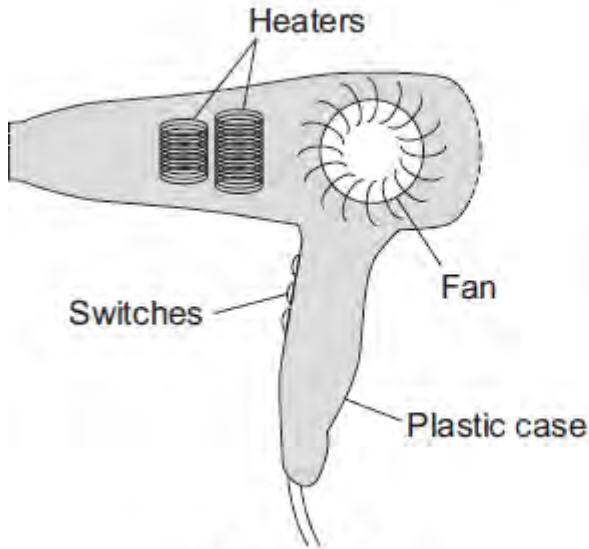


Diagram 1

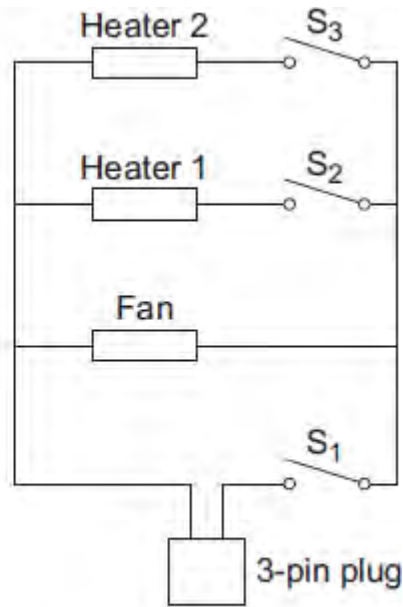


Diagram 2

(a) What colour is the insulation around the wire connected to the live pin inside the plug?

.....

(1)

(b) Why does the hairdryer **not** need an earth wire?

.....

(1)

(c) All the switches are shown in the OFF position.

(i) Which switch or switches have to be ON to make:

(1) only the fan work;

(2) heater 2 work?

(2)

- (ii) The heaters can only be switched on when the fan is also switched on.
Explain why.

.....

.....

.....

.....

.....

(2)

- (d) The table shows the current drawn from the 230 volt mains electricity supply when different parts of the hairdryer are switched on.

	Current in amps
Fan only	1.0
Fan and heater 1	4.4
Fan and both heaters	6.5

Calculate the maximum power of the hairdryer.

Show clearly how you work out your answer and give the unit.


.....

.....

Maximum power =

(3)
(Total 9 marks)

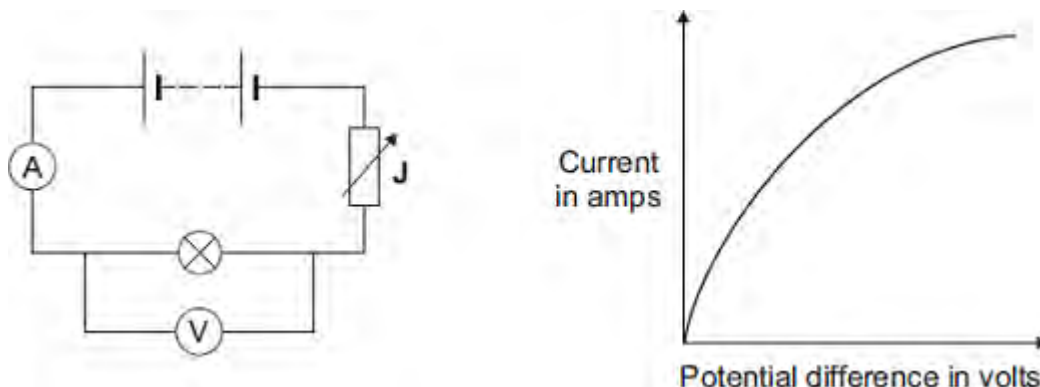Q3.(a) The diagram shows the circuit used to obtain the data needed to plot the current–potential difference graph for a filament bulb.



(i) Why is the component labelled 'J' included in the circuit?

.....

(1)

(ii) The resistance of the bulb increases as the potential difference across the bulb increases. Why?

.....

(1)

(iii) The bulb is at full brightness when the potential difference across the bulb is 12 V.
 The current through the bulb is then 3 A.

Calculate the power of the bulb when it is at full brightness and give the unit.

.....

Power =

(3)

(b) *In this question you will be assessed on using good English, organising information*

clearly and using specialist terms where appropriate.

The table gives data about two types of light bulb people may use in their homes.

Type of light bulb	Energy efficiency	Cost of one light bulb	Average lifetime in hours
Halogen	10%	£1.95	2 000
Light Emitting Diode (LED)	32%	£11.70	36 000

Both types of light bulb produce the same amount of light.

Evaluate, in terms of cost and energy efficiency, the use of the two types of light bulb.

To gain full marks you must compare both types of light bulb and conclude which light bulb would be the best to use.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(6)
(Total 11 marks)

Q4. If a fault develops in an electrical circuit, the current may become too great. The circuit needs to be protected by being disconnected.

A fuse or a circuit breaker may be used to protect the circuit.
One type of circuit breaker is a Residual Current Circuit Breaker (RCCB).

(a) (i) Use the correct answer from the box to complete the sentence.

earth	live	neutral
--------------	-------------	----------------

A fuse is connected in the wire.

(1)

(ii) Use the correct answer from the box to complete the sentence.

are bigger	are cheaper	react faster
-------------------	--------------------	---------------------

RCCBs are sometimes preferred to fuses because they

(1)

(iii) RCCBs operate by detecting a difference in the current between two wires.

Use the correct answer from the box to complete the sentence.

earth and live	earth and neutral	live and neutral
-----------------------	--------------------------	-------------------------


The two wires are the wires.

(1)

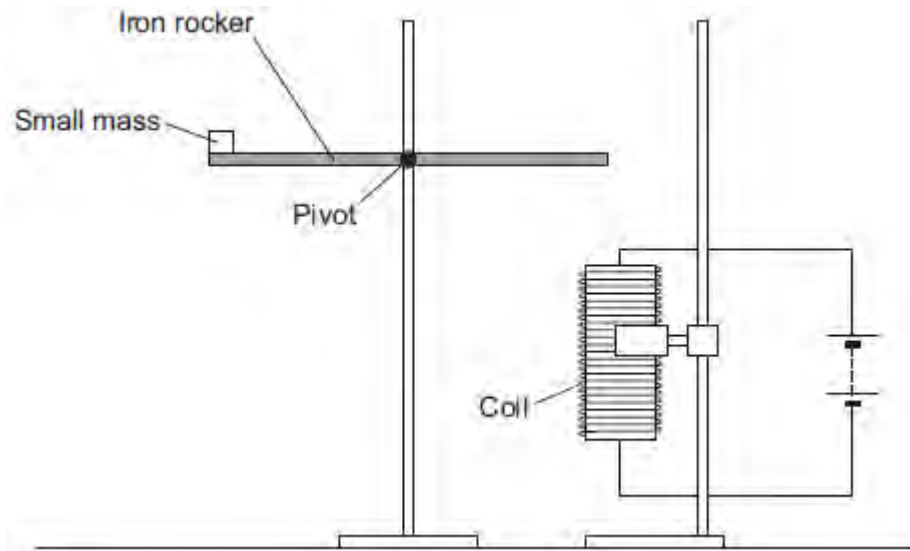(b) An RCCB contains an iron rocker and a coil.

A student investigated how the force of attraction, between a coil and an iron rocker, varies with the current in the coil.

She supported a coil vertically and connected it in an electrical circuit, part of which is shown in the figure below .



She put a small mass on the end of the rocker and increased the current in the coil until the rocker balanced. She repeated the procedure for different masses.

Some of her results are shown in the table below.

Mass in grams	Current needed for the rocker to balance in amps
5	0.5
10	1.0
15	1.5
20	2.0

- (i) State **two** extra components that must have been included in the circuit in the figure above to allow the data in the above table to be collected.

Give reasons for your answers.

.....

.....

.....

.....

.....

.....

.....

.....

(4)

(ii) A teacher said that the values of current were too high to be safe.

Suggest **two** changes that would allow lower values of current to be used in this investigation.

Change 1

.....

Change 2

.....

(2)

(Total 9 marks)

Q5.(a) A company is developing a system which can heat up and melt ice on roads in the winter. This system is called 'energy storage'.

During the summer, the black surface of the road will heat up in the sunshine.

This energy will be stored in a large amount of soil deep under the road surface. Pipes will run through the soil. In winter, cold water entering the pipes will be warmed and brought to the surface to melt ice.

The system could work well because the road surface is black.

Suggest why.

.....
.....

(1)

(b) (i) What is meant by specific latent heat of fusion?

.....
.....
.....
.....

(2)

(ii) Calculate the amount of energy required to melt 15 kg of ice at 0 °C.

Specific latent heat of fusion of ice = 3.4×10^5 J/kg.

.....
.....


Energy = J

(2)

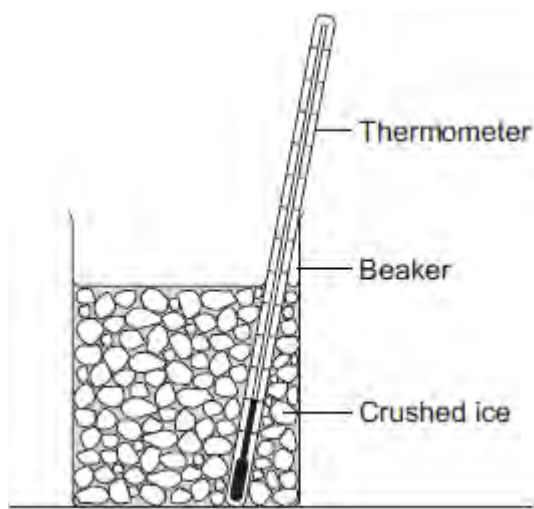(c) Another way to keep roads clear of ice is to spread salt on them. When salt is added to ice, the melting point of the ice changes.

A student investigated how the melting point of ice varies with the mass of salt added.

The figure below shows the equipment that she used.



The student added salt to crushed ice and measured the temperature at which the ice melted.

- (i) State **one** variable that the student should have controlled.

.....

(1)

- (ii) During the investigation the student stirred the crushed ice.

Suggest **two** reasons why.

Tick (✓) **two** boxes.

	Tick (✓)
To raise the melting point of the ice	
To lower the melting point of the ice	
To distribute the salt throughout the ice	
To keep all the ice at the same temperature	
To reduce energy transfer from the surroundings to the ice	

(2)

(iii) The table below shows the data that the student obtained.

Mass of salt added in grams	0	10	20
Melting point of ice in °C	0	-6	-16

Describe the pattern shown in the table.

.....
.....

(1)

(d) Undersoil electrical heating systems are used in greenhouses. This system could also be used under a road.

A cable just below the ground carries an electric current. One greenhouse system has a power output of 0.50 kW.

Calculate the energy transferred in 2 minutes.

.....
.....
.....

Energy transferred = J

(3)

(e) **In this question you will be assessed on using good English, organising information clearly and using specialist terms where appropriate.**

A local council wants to keep a particular section of a road clear of ice in the winter.

Describe the advantages and disadvantages of keeping the road clear of ice using:

- energy storage
- salt
- undersoil electrical heating.

.....

- M1.** (a) (because the) potential of the live wire is 230 V 1
- (and the) potential of the electrician is 0 V 1
- (so there is a) large potential difference between live wire and electrician 1
- charge / current passes through his body
allow voltage for potential difference 1
- (b) diameter between 3.50 and 3.55 (mm)
allow correct use of value of cross-sectional area of 9.5 to 9.9 (mm²) with no final answer given for 1 mark 2
- (c) $18000 = I \times 300$ 1
- $I = 18000 / 300 = 60$ 1
- $13\,800 = (60^2) \times R$ 1
- $R = 13\,800 / 60^2$ 1
- 3.83 (Ω) 1

*allow 3.83(Ω) with no working shown for 5 marks
answer may also be correctly calculated using $P = IV$ and $V = IR$ if 230 V is used.*

[11]

M2. (a) 35

an answer with more than 2 sig figs that rounds to 35 gains 2 marks

allow 2 marks for correct method, ie $\frac{230}{6.5}$

allow 1 mark for $I = 6.5$ (A) or $R = \frac{230}{26}$

an answer 8.8 gains 2 marks

an answer with more than 2 sig figs that rounds to 8.8 gains 1 mark

3

- (b) (maximum) current exceeds maximum safe current for a 2.5 mm² wire
accept power exceeds maximum safe power for a 2.5 mm² wire

or(maximum) current exceeds 20 (A)
(maximum) current = 26 (A) is insufficient

1

a 2.5 mm² wire would overheat / melt
accept socket for wire
*do **not** accept plug for wire*

1

- (c) a.c. is constantly changing direction
accept a.c. flows in two directions
accept a.c. changes direction
a.c. travels in different directions is insufficient

1

d.c. flows in one direction only

1

[7]

M3. (a) water heated by radiation (from the Sun)
accept IR / energy for radiation 1

water used to heat buildings / provide hot water
allow for 1 mark heat from the Sun heats water if no other marks given
references to photovoltaic cells / electricity scores 0 marks 1

(b) 2 (minutes)
$$1.4 \times 10^3 = \frac{168 \times 10^3}{t}$$
gains 1 mark
calculation of time of 120 (seconds) scores 2 marks 3

(c) (i) 150 (kWh) 1

(ii) £60(.00) or 6000 (p)
an answer of £6000 gains 1 mark
allow 1 mark for $150 \times 0.4(0)$ 150×40
allow ecf from (c)(i) 2

(iii) 25 (years)
an answer of $6000 / 240$
or
 $6000 / \text{their (c)(ii)} \times 4$
gains 2 marks
an answer of $6000 / 60$
or
 $6000 / \text{their (c)(ii)}$ gains 1 mark, ignore any other multiplier of (c)(ii) 3

(iv) any **one** from:

- will get £240 per year
accept value consistent with calculated value in (c)(iii)
- amount of light is constant throughout the year
- price per unit stays the same
- condition of cells does not deteriorate

1

(d) any **one** from:

- angle of tilt of cells
- cloud cover
- season / shade by trees
- amount of dirt

1

[13]

M4. (a) attempt to draw four cells in series

1

correct circuit symbols

circuit symbol should show a long line and a short line,
correctly joined together

example of correct circuit symbol:



1

(b) (i) 6 (V)

allow 1 mark for correct substitution, ie

$V = 3 \times 2$ scores 1 mark

provided no subsequent step

2

(ii) 12 (V)

ecf from part (b)(i)

$18 - 6$

or

$18 -$ their part (b)(i) scores 1 mark

2

(iii) 9 (Ω)

ecf from part (b)(ii) correctly calculated

$3 +$ their part (b)(ii) / 2

or

$18 / 2$ scores 1 mark

provided no subsequent step

2

(c) (i) need a.c.

1

battery is d.c.

1

(ii) 3 (A)

*allow 1 mark for correct substitution, ie
 $18 \times 2 = 12 \times I_s$, scores 1 mark*

2

[12]

- M5.** (a) (i) generator 1
- (ii) alternating current 1
- (iii) voltmeter / CRO / oscilloscope / cathode ray oscilloscope 1
- (b) (i) time 1
- (ii) peaks and troughs in opposite directions 1
- amplitude remains constant
dependent on first marking point 1
- (c) any **two** from:
- increase speed of coil
 - strengthen magnetic field
 - increase area of coil
- do not accept larger* 2

[8]

Q1.An electrician is replacing an old electric shower with a new one.

The inside of the old shower is shown in **Figure 1**.

Figure 1



© Michael Priest

(a) If the electrician touches the live wire he will receive an electric shock.

Explain why.

.....

.....

.....

.....

.....

.....

.....

.....


.....

(4)

- (b) Different electrical wires need to have a cross-sectional area that is suitable for the power output.

Figure 2 shows the recommended maximum power input to wires of different cross-sectional areas.

Figure 2

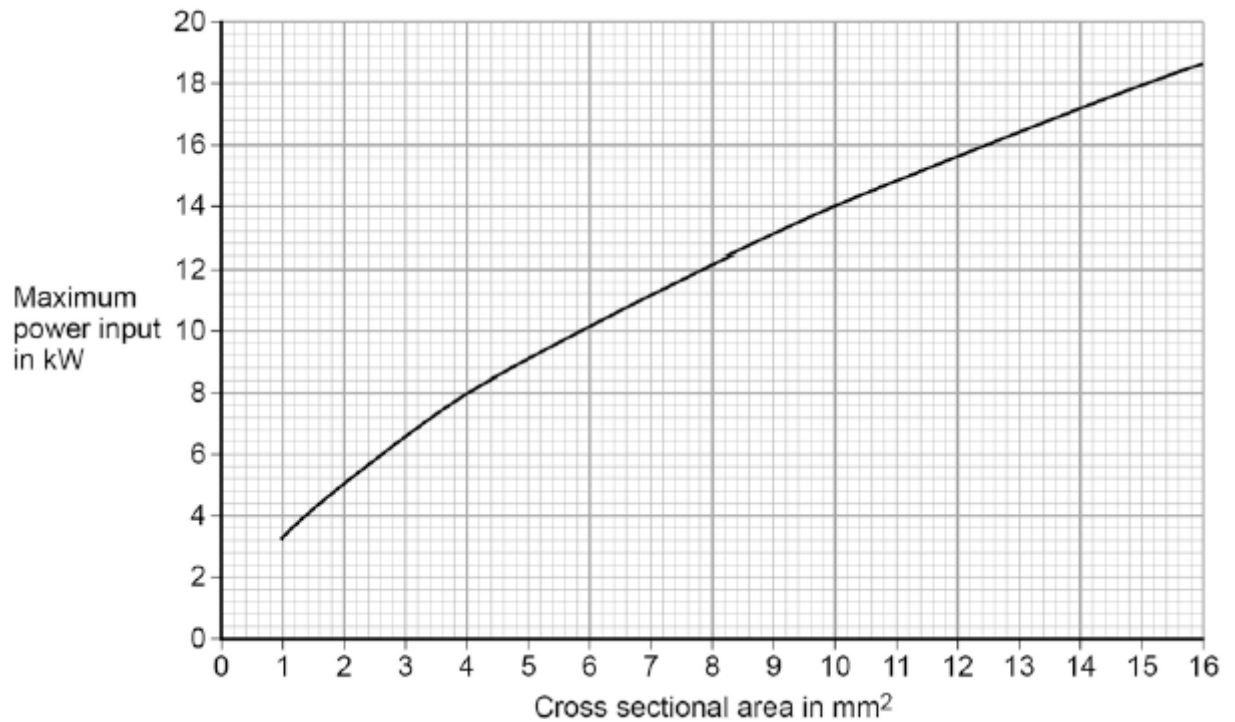

The new electric shower has a power input of 13.8 kW.

Determine the minimum **diameter** of wire that should be used for the new shower.

The diameter, d , can be calculated using the equation:

$$d = \sqrt{\frac{4A}{\pi}}$$

A is the cross-sectional area of the wire.

.....

Minimum diameter = mm

(2)

- (c) The charge that flows through the new shower in 300 seconds is 18 000 C.

The new electric shower has a power of 13.8 kW.

Calculate the resistance of the heating element in the new shower.


Write down any equations you use.

.....
.....
.....
.....
.....
.....
.....
.....

Resistance = Ω

(5)
(Total 11 marks)

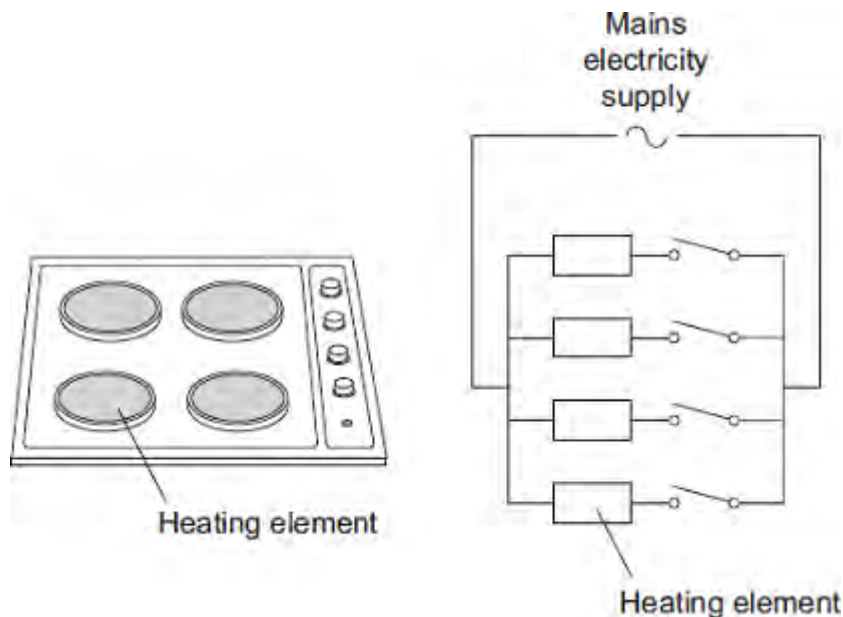Q2. The picture shows an electric cooker hob. The simplified circuit diagram shows how the four heating elements connect to the mains electricity supply. The heating elements are identical.



When all four heating elements are switched on at full power the hob draws a current of 26 A from the 230 V mains electricity supply.

- (a) Calculate the resistance of one heating element when the hob is switched on at full power.

Give your answer to 2 significant figures.

.....

.....

.....

Resistance = Ω

(3)

- (b) The table gives the maximum current that can safely pass through copper wires of different cross-sectional area.

Cross-sectional area in mm^2	Maximum safe current in amps
1.0	11.5
2.5	20.0

4.0	27.0
6.0	34.0

The power sockets in a home are wired to the mains electricity supply using cables containing 2.5 mm^2 copper wires. Most electrical appliances are connected to the mains electricity supply by plugging them into a standard power socket.

It would **not** be safe to connect the electric cooker hob to the mains electricity supply by plugging it into a standard power socket.

Why?

.....

.....

.....

.....

(2)

- (c) Mains electricity is an alternating current supply. Batteries supply a direct current.

What is the difference between an alternating current and a direct current?

.....

.....

.....

.....

(2)

(Total 7 marks)

Q3. Solar panels are often seen on the roofs of houses.

(a) Describe the action and purpose of a solar panel.


.....
.....
.....
.....

(2)

(b) Photovoltaic cells transfer light energy to electrical energy.

In the UK, some householders have fitted modules containing photovoltaic cells on the roofs of their houses.

Four modules are shown in the diagram.

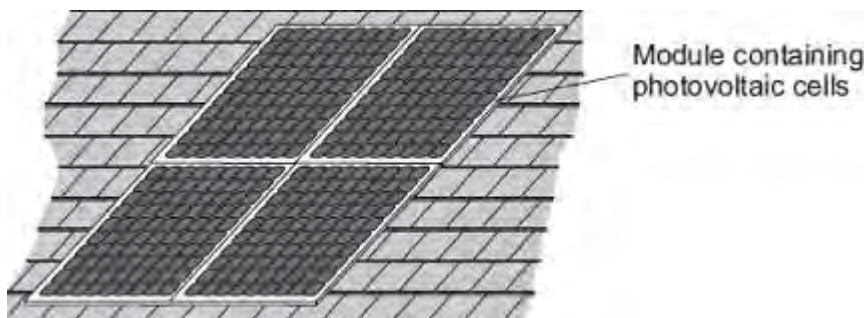

The electricity company pays the householder for the energy transferred.

The maximum power available from the photovoltaic cells shown in the diagram is 1.4×10^3 W.

How long, in minutes, does it take to transfer 168 kJ of energy?

.....
.....
.....
.....
.....
.....
..... Time = minutes

(3)

(c) When the modules are fitted on a roof, the householder gets an extra electricity meter to measure the amount of energy transferred by the photovoltaic cells.

(i) The diagram shows two readings of this electricity meter taken three months apart.
The readings are in kilowatt-hours (kWh).

21 November

0	0	0	4	4
---	---	---	---	---

21 February

0	0	1	9	4
---	---	---	---	---

Calculate the energy transferred by the photovoltaic cells during this time period.

.....

Energy transferred = kWh

(1)

(ii) The electricity company pays 40p for each kWh of energy transferred.

Calculate the money the electricity company would pay the householder.

.....

.....

Money paid =

(2)

(iii) The cost of the four modules is £6000.

Calculate the payback time in years for the modules.

.....

.....

Payback time = years

(3)

(iv) State an assumption you have made in your calculation in part (iii).

.....
.....

(1)

(d) In the northern hemisphere, the modules should always face south for the maximum transfer of energy.

State **one** other factor that would affect the amount of energy transferred during daylight hours.

.....
.....

(1)

(Total 13 marks)

Q4. The current in a circuit depends on the potential difference (p.d.) provided by the cells and the total resistance of the circuit.

- (a) Using the correct circuit symbols, draw a diagram to show how you would connect 1.5 V cells together to give a p.d. of 6 V.


(2)

- (b) **Figure 1** shows a circuit containing an 18 V battery.

Two resistors, **X** and **Y**, are connected in series.

- **X** has a resistance of 3Ω .
- There is a current of 2 A in **X**.

Figure 1

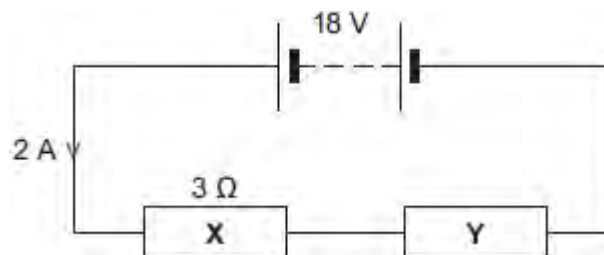

- (i) Calculate the p.d. across **X**.

.....

P.d. across **X** = V

(2)

- (ii) Calculate the p.d. across **Y**.

.....

P.d. across **Y** = V

(2)

(iii) Calculate the total resistance of X and Y.


.....
.....
.....

Total resistance of X and Y = Ω

(2)

(c) **Figure 2** shows a transformer.

Figure 2

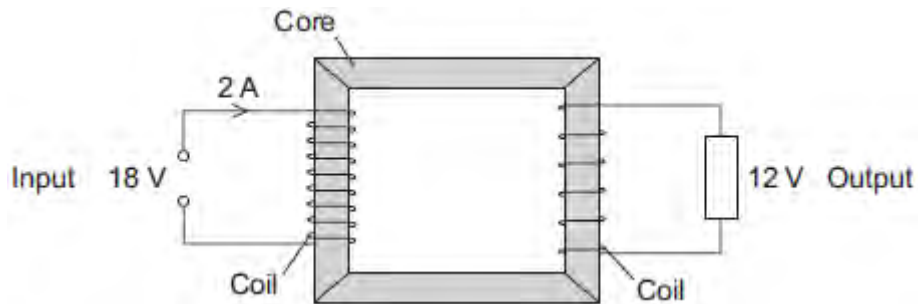

(i) An 18 V battery could **not** be used as the input of a transformer.

Explain why.

.....
.....
.....
.....

(2)

(ii) The transformer is 100% efficient.

Calculate the output current for the transformer shown in **Figure 2**.


.....
.....
.....

Output current = A

(2)
(Total 12 marks)

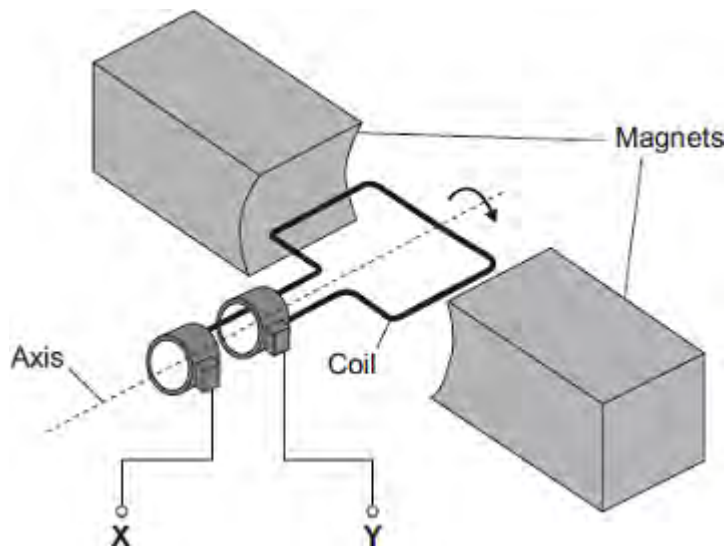Q5.The diagram shows an a.c. generator.

The coil rotates about the axis shown and cuts through the magnetic field produced by the magnets.



- (a) (i) A potential difference is induced between **X** and **Y**.

Use the correct answer from the box to complete the sentence.

electric	generator	motor	transformer
-----------------	------------------	--------------	--------------------

This effect is called the effect.

(1)

- (ii) What do the letters a.c. stand for?

.....

(1)


- (iii) Name an instrument that could be used to measure the potential difference between **X** and **Y**.

.....

(1)

- (b) **Graph 1** shows the output from the a.c. generator.

Graph 1

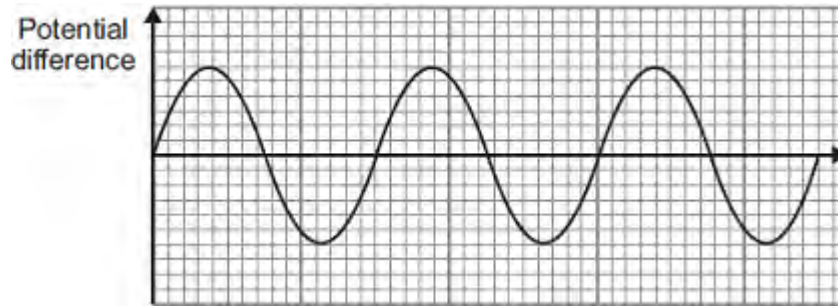

- (i) One of the axes on **Graph 1** has been labelled 'Potential difference'.
What should the other axis be labelled?

.....

(1)

- (ii) The direction of the magnetic field is reversed.

On **Graph 1**, draw the output from the a.c. generator if everything else remains the same.

(2)

- (c) The number of turns of wire on the coil is increased. This increases the maximum induced potential difference.

State **two** other ways in which the maximum induced potential difference could be increased.

1

.....

2

.....

(2)

(Total 8 marks)

M1.	<p>(a) Level 2 (3–4 marks): A detailed and coherent explanation is provided. The student makes logical links between clearly identified, relevant points.</p> <p>Level 1 (1–2 marks): Simple statements are made, but not precisely. The logic is unclear.</p> <p>0 marks: No relevant content</p> <p>Indicative content</p> <ul style="list-style-type: none"> • friction (between cloth and rod) causes • electrons (to) move • from the acetate rod or to the cloth • (net) charge on cloth is now negative • (net) charge on rod is now positive 	4
	<p>(b) there is a force of attraction between the acetate rod and the cloth</p> <p>(reason)</p> <p>unlike charges attract</p> <p>or</p> <p>negative charges attract positive charges</p>	1
	<p>(c) increase</p>	1
	<p>(d) $0.000025 \times 60\,000$</p> <p>1.5 (J)</p>	1

accept 1.5 (J) with no working shown for 2 marks

[9]

- M2.** (a) (i) (bottom **or** other ends) move apart or
repel
accept they move apart 1
- (ii) have same charge
accept both have negative charge
(from part (b) do not credit both have positive charge
same **or** like charges repel
not just opposite charges attract 2
- (b) positive 1
- electrons 1
- cloth 1
- polythene
accept strips 1
- (c) (i) conductors
accept metals 1
- (ii) insulators
accept non-conductors/poor conductors do not credit
non-metals 1

[9]

M3. (a) becomes (electrically) charged or description of electron movement
for 1 mark

1

(b) comb attracts paper
for 1 mark

1

(c) charge/electricity gone to Earth/body
for 1 mark each

2

[4]

- M4.** (a) (i) electrons 1
- jumper 1
- (ii) positive 1
accept protons
accept +
- (iii) positively charged 1
accept any clear way of indicating the answer
- (b) (i) copper 1
- it is an (electrical) conductor
only accept if copper is identified
*do **not** accept it conducts heat*
accept it conducts heat and electricity
accept copper is the best conductor
accept correct description of conduction 1
- (ii) current 1

[7]

- M5.** (a) repel 1
- opposite 1
- attract 1
- correct order only*
- (b) refuelling an aircraft 1
- reason cannot score if refuelling aircraft is not chosen*
- a spark may cause an explosion / fire / ignite the fuel
- accept the static for a spark*
- accept named fuel*
- there must be a consequence of having a spark*
- do **not** accept answers in terms of people getting a shock or electrocuted*
- 1

[5]

M6. (a) (i) electrons 1

a positive 1

(ii) (forces are) equal
accept (forces are) the same
forces are balanced is insufficient 1

(forces act in) opposite directions
accept (forces) repel
both sides have the same charge is insufficient 1

(b) aluminium 1

[5]

M7. (a) fleece rubs against shirt
it refers to the fleece 1

or
friction (between fleece and shirt)
(causing) electrons to transfer from one to the other
accept a specific direction of transfer
*do **not** accept charge for electrons*
positive electrons negates this mark
movement of protons negates this mark 1

(b) Electrical charges move easily through metals. 1

An electric current is a flow of electrical charge. 1

(c) (i) copper
reason only scores if copper chosen 1

(good electrical) conductor
accept it is a metal
any mention of heat conduction negates this mark 1

(ii) lower than 1

(iii) accept any sensible suggestion, eg:
• too many variables (to control)
• lightning strikes / storms are random / unpredictable


- do not know which building will be struck
- do not know when a building will be struck
- do not know when lightning will happen
- (very) difficult to create same conditions in a laboratory
- lightning storms are not the same
 - it is not safe is insufficient*
 - do **not** accept lightning does not strike the same place twice*

1

[8]

Q1.A student rubs an acetate rod with a cloth.

Figure 1 shows the charges on the acetate rod and cloth before and after rubbing.

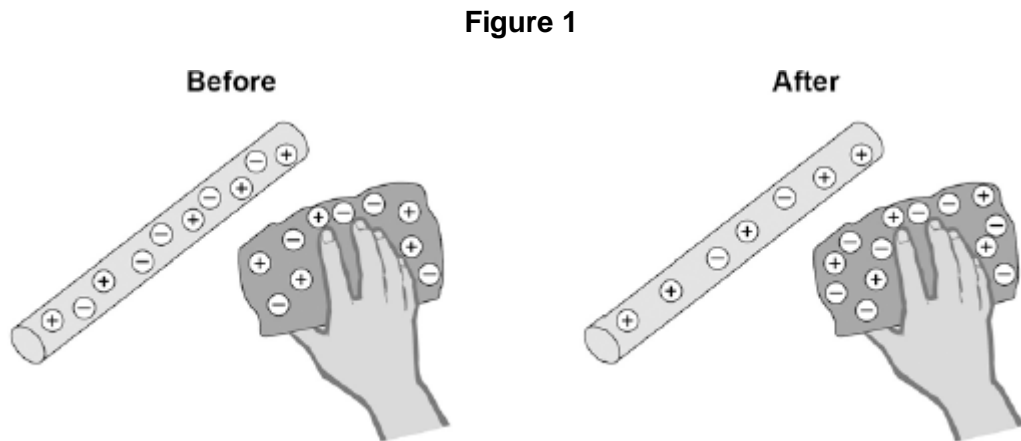

- (a) Explain how rubbing an acetate rod with a cloth causes the rod and cloth to become charged.

.....

.....

.....

.....

.....

.....

.....

.....

(4)

- (b) After charging them, the student moves the acetate rod and the cloth closer together.

Which statement is correct?

Tick **one** box.

There is no force between the acetate rod and the cloth.

There is a force of attraction between the acetate rod and the cloth.

There is a force of repulsion between the acetate rod and the cloth.



Give a reason for your answer.

.....


.....

.....

(2)

- (c) **Figure 2** shows a Van de Graaff generator, which is used to generate static electricity.

Figure 2

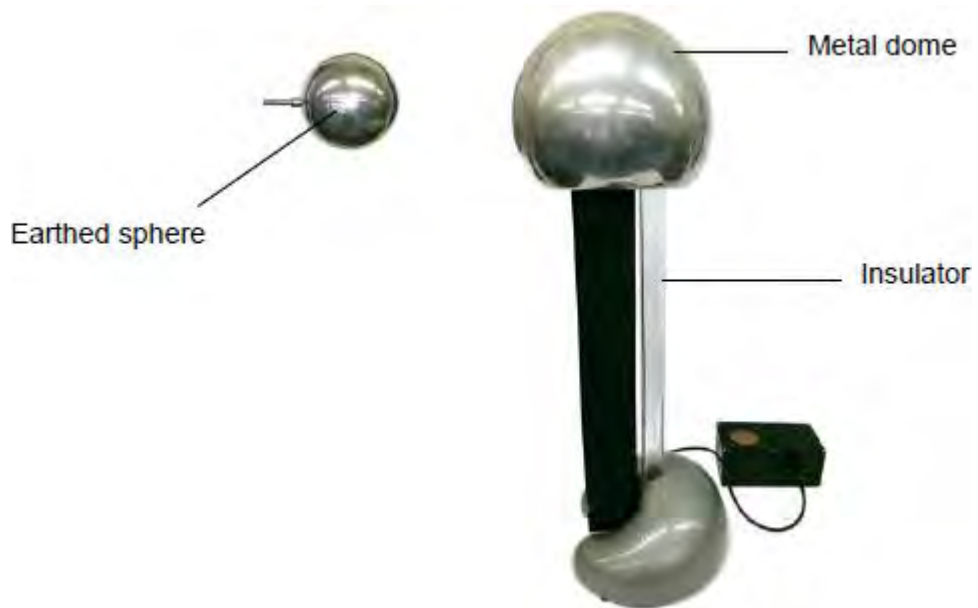

© Michael Priest

The longer the Van de Graaff generator is switched on, the more charge is stored on the metal dome.

Use an answer from the box to complete the sentence.

decrease	increase	stay the
	same	

The amount of charge on the metal dome is increased, which causes the potential

difference between the metal dome and the earthed sphere to

.....

(1)

- (d) When the potential difference between the Van de Graaff generator and the earthed sphere is 60 kV, a spark jumps between the metal dome and the earthed sphere.

The spark transfers 0.000025 coulombs of charge to the earthed sphere.

The equation which links charge, energy and potential difference is:

$$\text{energy transferred} = \text{charge} \times \text{potential difference}$$

Calculate the energy transferred by the spark.

.....
.....
.....

Energy transferred = J

(2)

(Total 9 marks)

Q2. A student did an experiment with two strips of polythene. She held the strips together at one end. She rubbed down one strip with a dry cloth. Then she rubbed down the other strip with the dry cloth. Still holding the top ends together, she held up the strips.



(a) (i) What movement would you expect to see?

.....
.....

(1)

(ii) Why do the strips move in this way?

.....

(2)

(b) Complete the **four** spaces in the passage.

Each strip has a negative charge. The cloth is left with a.....
charge. This is because particles called have been transferred
from the to the

(4)

- (c) The student tried the experiment using two strips of aluminium. The strips did not move.

Complete **each** of the sentences.

- (i) Materials, such as aluminium, which electricity will pass through easily, are called

(1)

- (ii) Materials, such as polythene which electricity will **not** pass through easily, are called

(1)

(Total 9 marks)

Q3. You wash and dry your hair, then comb it with a plastic comb. As you move the comb away from your head some hairs are attracted to the comb.

(a) What has happened to the comb to make it attract the hairs?

.....
.....

(1)

(b) If the comb is now held above some small pieces of dry tissue paper what is likely to happen?

.....
.....

(1)

(c) If you rub your hands all over the comb it will no longer attract your hair. Explain why.

.....
.....

(2)

(Total 4 marks)

Q4. (a) A student rubs a nylon comb on the sleeve of his jumper.



(i) Use words from the box to complete the following sentence.

electrons	hand	jumper	protons
------------------	-------------	---------------	----------------

The comb becomes negatively charged because
move
from the student's to the comb.

(2)

(ii) What type of charge is left on the jumper?

.....

(1)

(iii) The negatively charged comb is placed close to a charged plastic ruler. The comb and the ruler attract each other.


Complete the following sentence by drawing a ring around the correct line in the box.

The ruler is

negatively charged
positively charged
uncharged

(1)

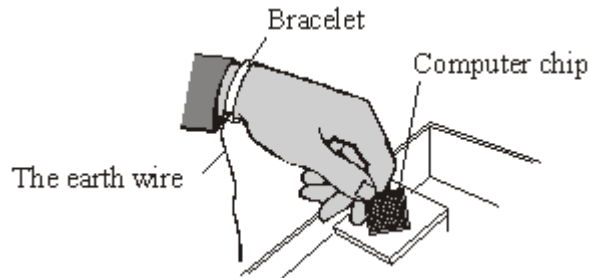- (b) Electrostatic charge can damage computer chips. People working with computer chips may wear a special bracelet, with a wire joining the bracelet to earth (the earth wire). Any negative charge on the person will flow through the wire to earth.



- (i) Which **one** of the following materials should the bracelet be made from?

Draw a ring around your answer.

copper plastic rubber

Give a reason for your answer.

.....
.....

(2)

- (ii) Which **one** of the following words is used to describe the rate of flow of charge through a wire?


Draw a ring around your answer.

current resistance voltage

(1)

(Total 7 marks)

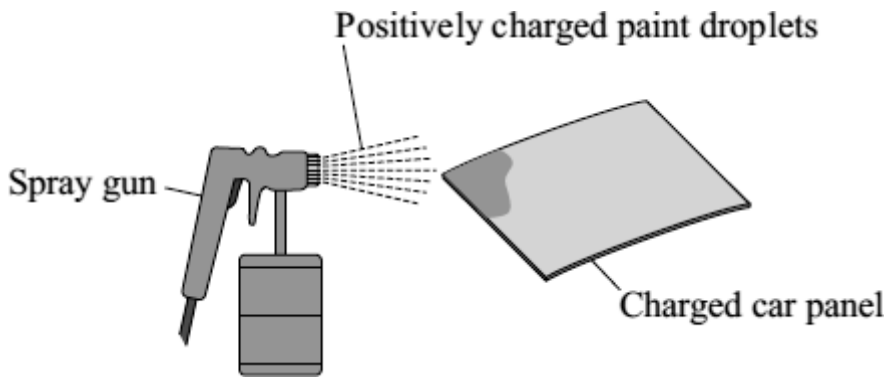Q5. (a) The diagram shows how static electricity is used to paint a metal car panel.



Use words from the box to complete the following sentences.

attract	opposite	repel	same
---------	----------	-------	------

All the paint droplets have the same type of charge. This makes the paint droplets each other and spread out.

The car panel and the paint droplets have the type of

charge. This causes the car panel to the paint droplets.

The car panel is covered by an even layer of paint.

(3)

(b) In which **one** of the following situations is static electricity dangerous and not useful?

Put a tick (✓) in the box next to your answer.


- using a photocopier
- refuelling an aircraft
- a smoke precipitator

Give a reason for your answer.

.....
.....

(2)
(Total 5 marks)

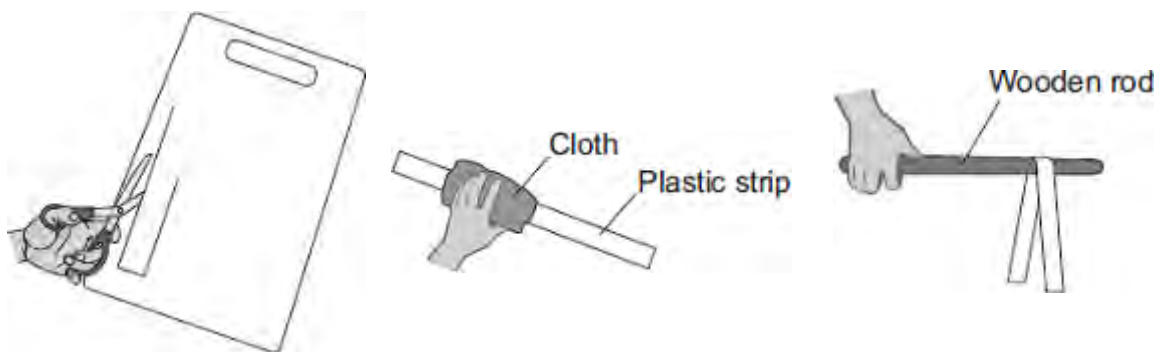Q6.(a) A student uses some everyday items to investigate static electricity.



- 1 A strip of plastic is cut from a plastic carrier bag 2 The plastic strip is rubbed with a cloth 3 The plastic strip is hung over a wooden rod

(i) Draw a ring around the correct answer in the box to complete each sentence.

Rubbing the plastic strip with a cloth causes the strip to become negatively charged.

This happens because

electrons
neutrons
protons

 move from the cloth onto the plastic strip.

The cloth is left with

a negative
a positive
zero

 charge.

(2)

(ii) When the plastic strip is hung over the wooden rod, the two halves of the strip move equally away from each other.

What **two** conclusions should the student make about the forces acting on the two halves of the plastic strip?

1

.....

2

.....

(2)

- (b) Electrical charges move more easily through some materials than through other materials.

Through which **one** of the following materials would an electrical charge move most easily?

Draw a ring around your answer.

aluminium


glass

rubber

(1)

(Total 5 marks)

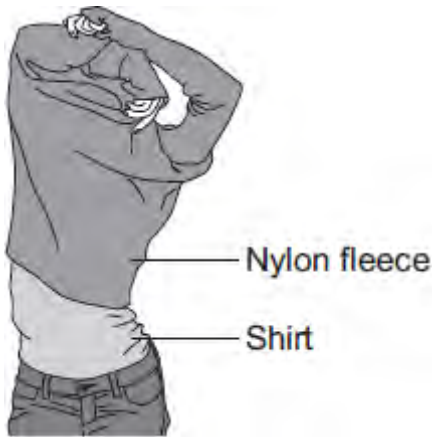- Q7.** (a) A student takes off his nylon fleece and feels a small electric shock. He realises that this happens because his fleece becomes charged.



Explain why the fleece becomes charged.

.....

.....

.....

.....

.....

(2)

- (b) Only **two** of the following statements are correct.

Put a tick (✓) in the boxes next to the **two** correct statements.

Positively charged objects repel negatively charged objects.

Electrical charges move easily through metals.


Static electricity is safe; it never causes any danger.

An electric current is a flow of electrical charge.



(2)

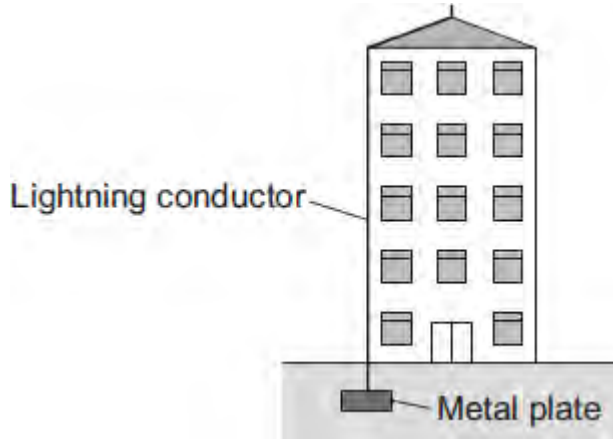(c) The diagram shows a lightning conductor attached to the side of a tall building.



If the building is struck by lightning, charge flows to earth through the lightning conductor.

(i) Which of the materials in the list is used to make the lightning conductor?

Draw a ring around your answer.

copper

glass

plastic

Give a reason for your answer.

.....
.....
.....

(2)

(ii) Complete the sentence by drawing a ring around the correct line in the box.

The resistance of the lightning conductor is

higher than

the same as the resistance of the building.
lower than

(1)

- (iii) It is almost impossible to test different designs of lightning conductor in controlled experiments during a lightning storm.

Suggest a reason why.

.....
.....

(1)

(Total 8 marks)